 


# Computer Architecture



Paul Mellies

Lecture 10 : Latches & Flip-Flops


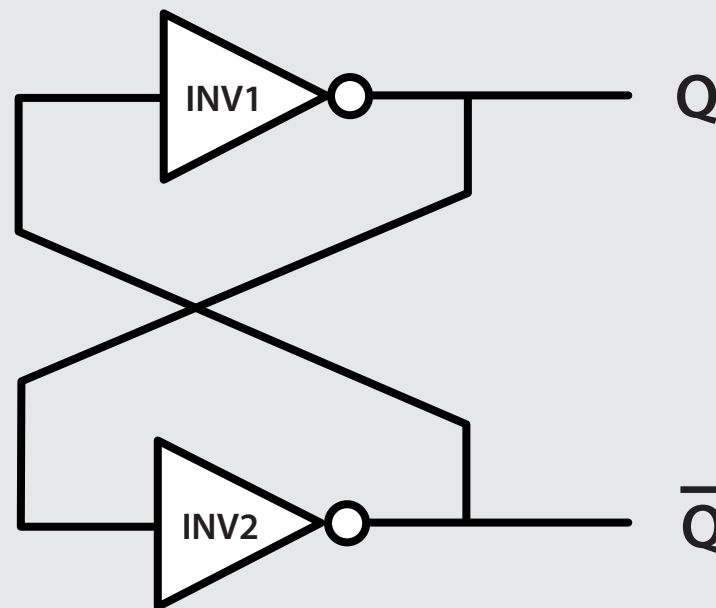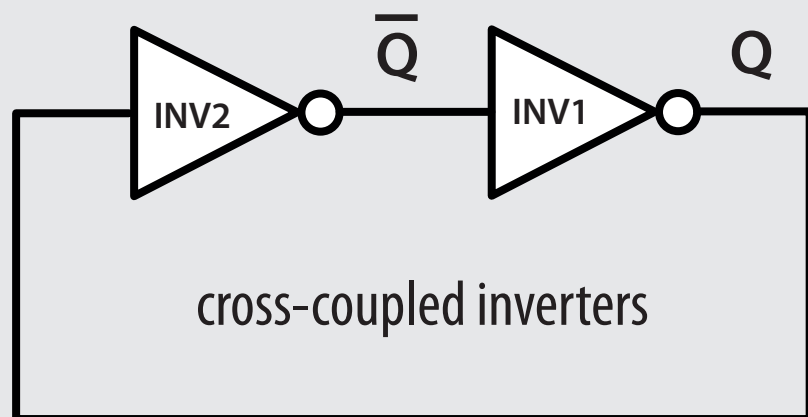
# Latches and flip-flops


The fundamental building block of memory is a *bistable* element, that is : an element with two stable states.




First stable state :  $Q = 0$  and  $\bar{Q} = 1$

Second stable state :  $Q = 1$  and  $\bar{Q} = 0$

# The two stable states

 

First stable state

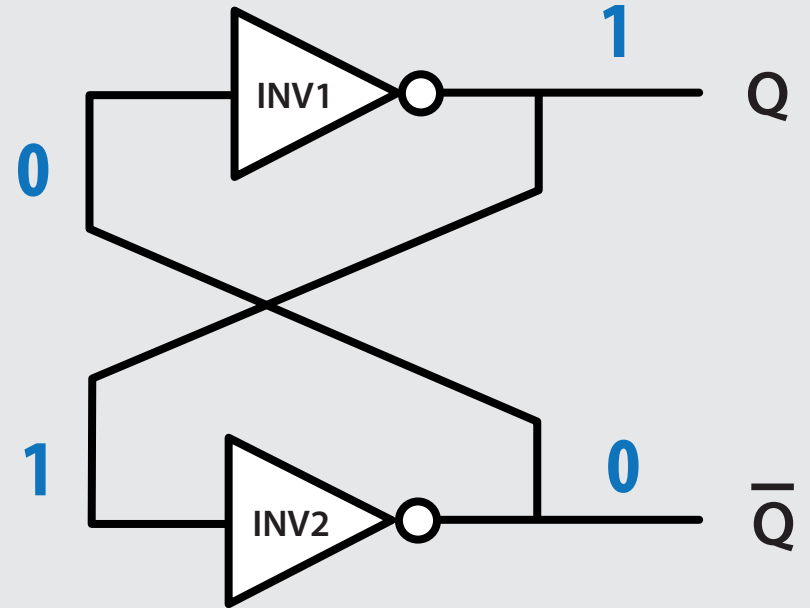


Second stable state

# SR latches
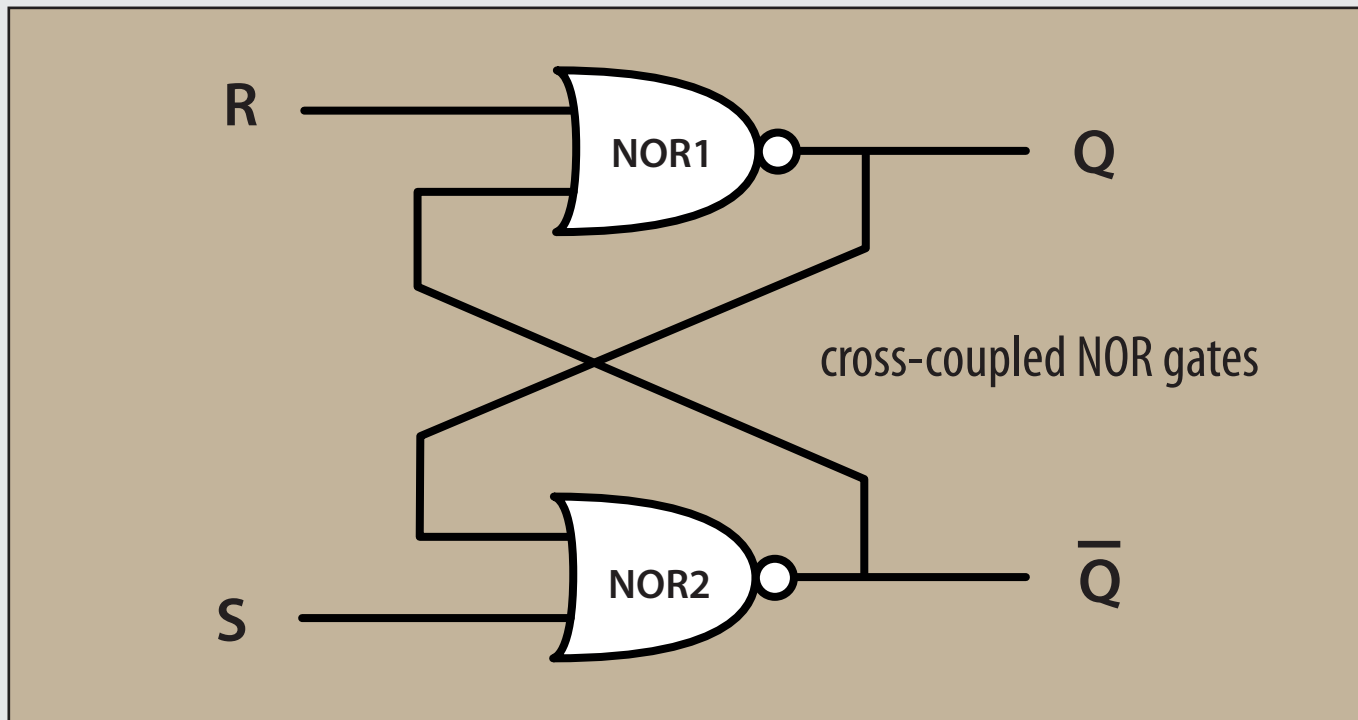
# SR-latches


The SR-latch is one of the simplest sequential circuits consisting of two cross-coupled NOR gates :



The SR-latch is similar to the cross-coupled inverters, except that its internal state can be controlled by the S and R inputs :


- S stands for *set*
- R stands for *reset*

# Two useful equalities to remember

 

# Application to the SR-latch


Set = 0 & Reset = 0

 

The SR-latch behaves as a pair of cross-coupled inverters.

# Application to the SR-latch


## Set = 1

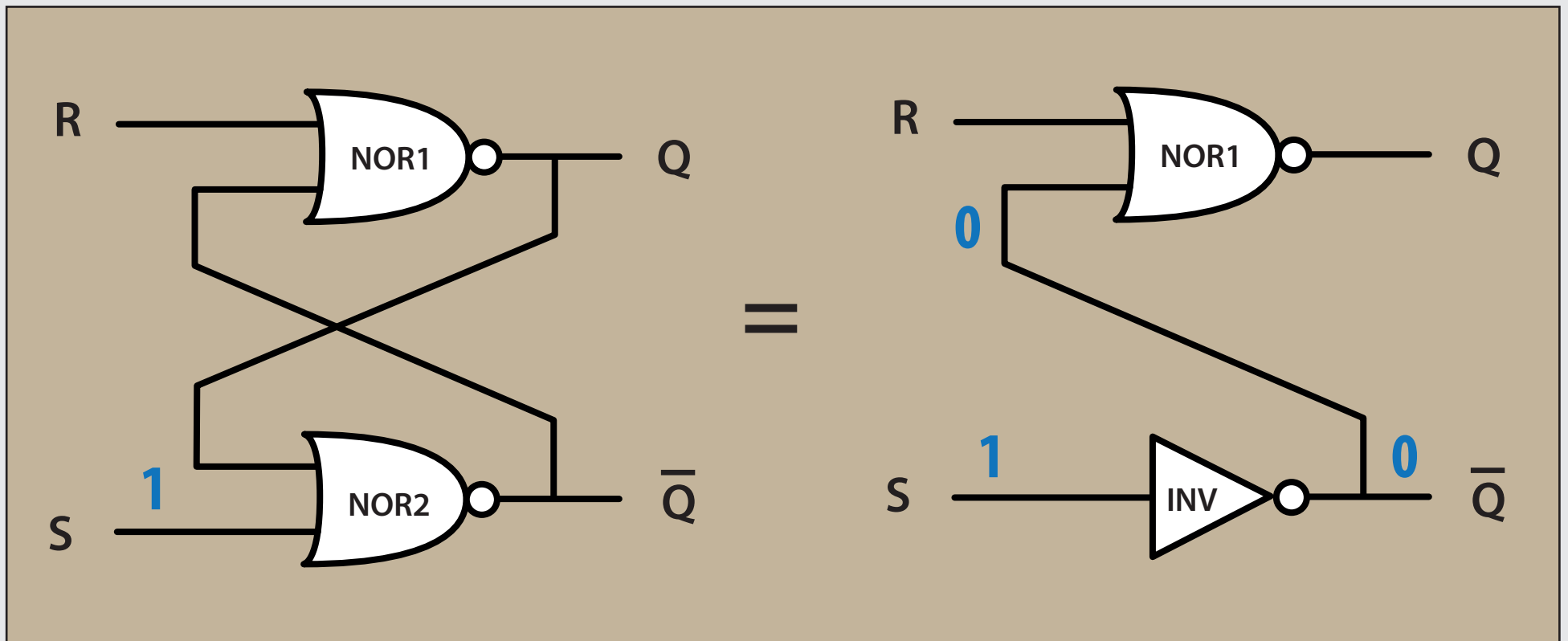




# Application to the SR-latch

## Set = 1

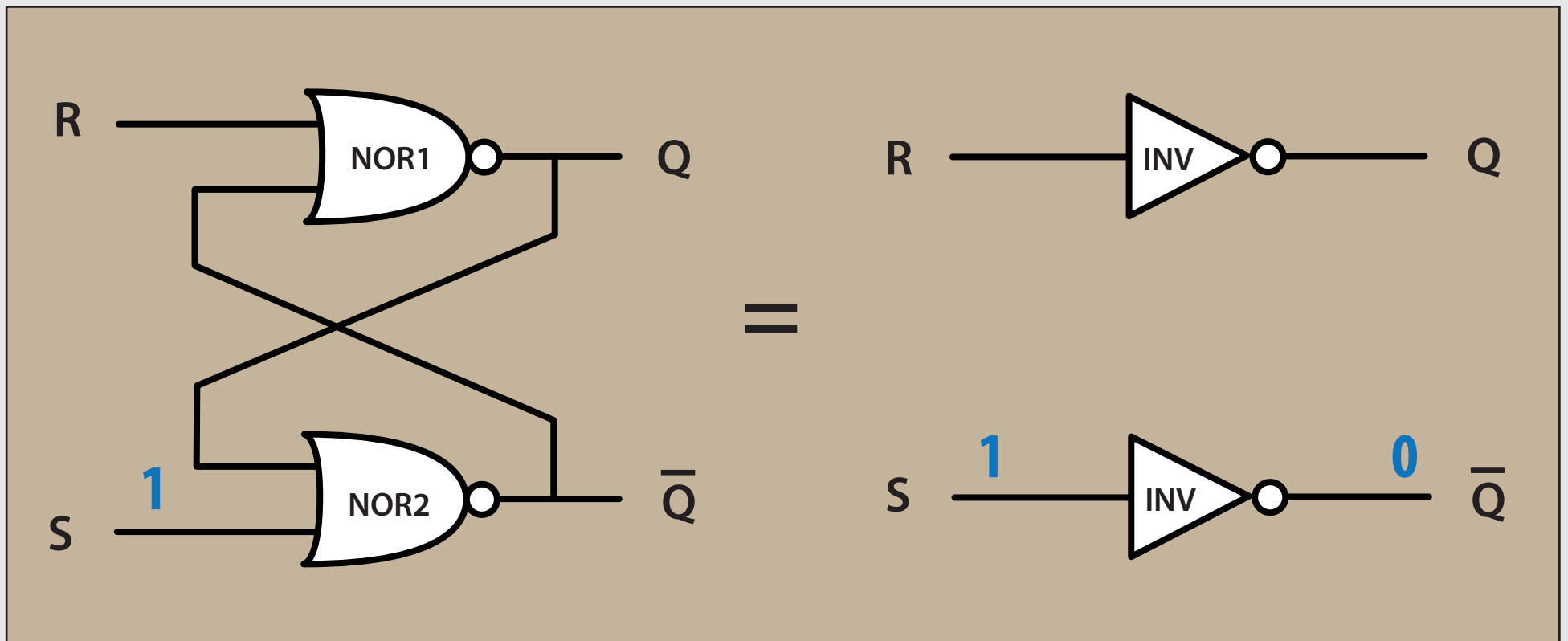


# Application to the SR-latch

Set = 1 & Reset = 0

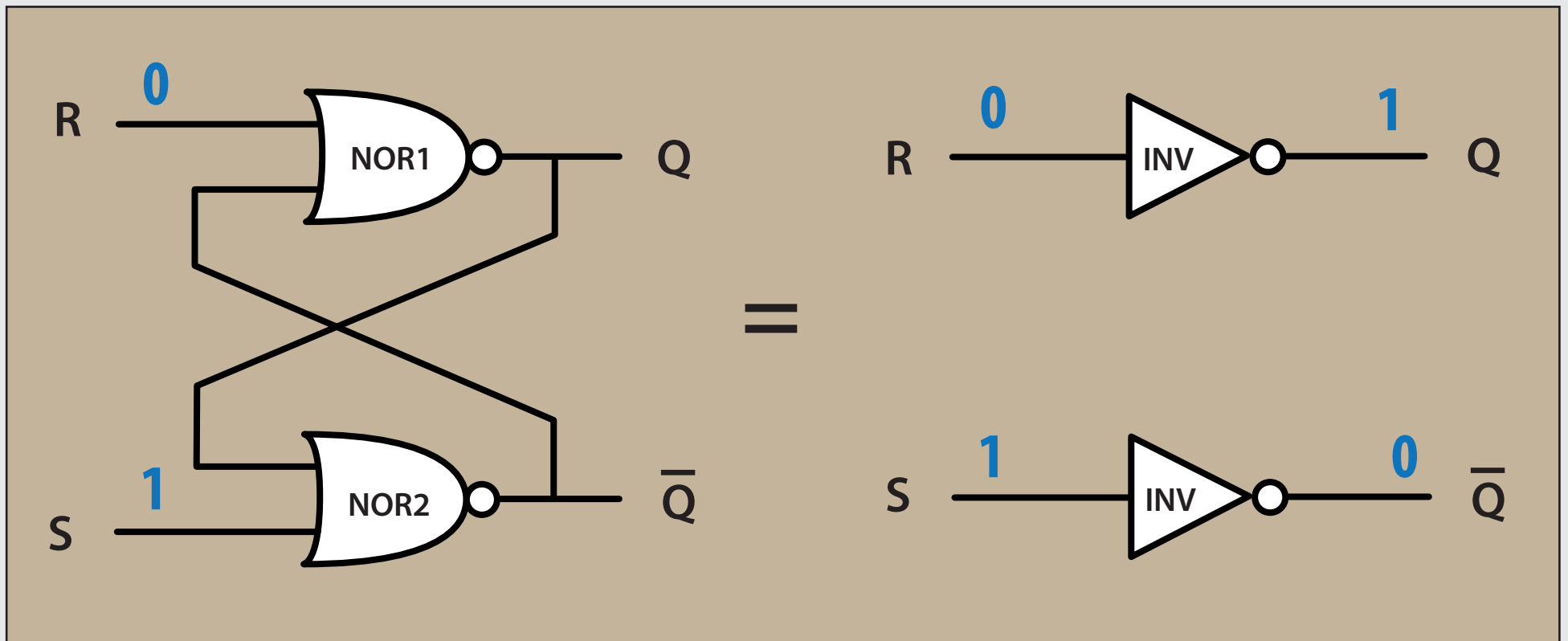


# Application to the SR-latch

Set = 0 & Reset = 1

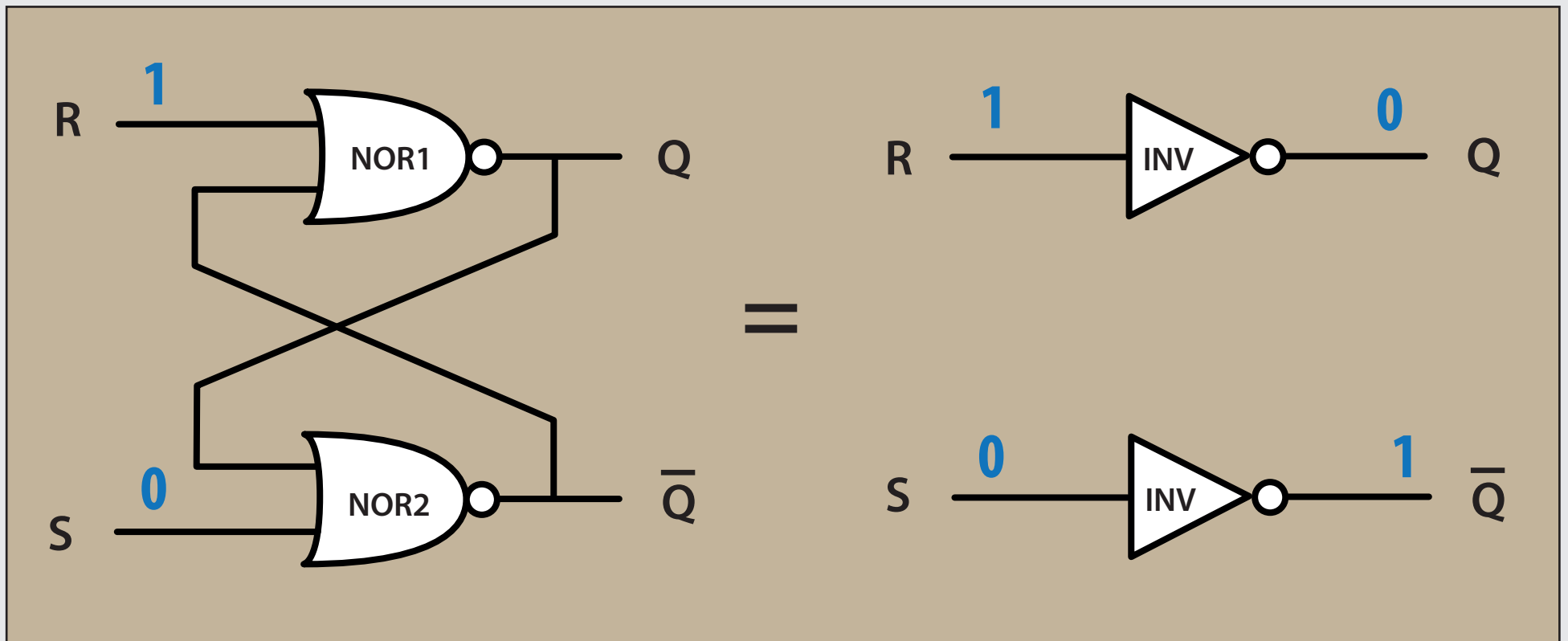

# Application to the SR-latch

Set = 1 & Reset = 1

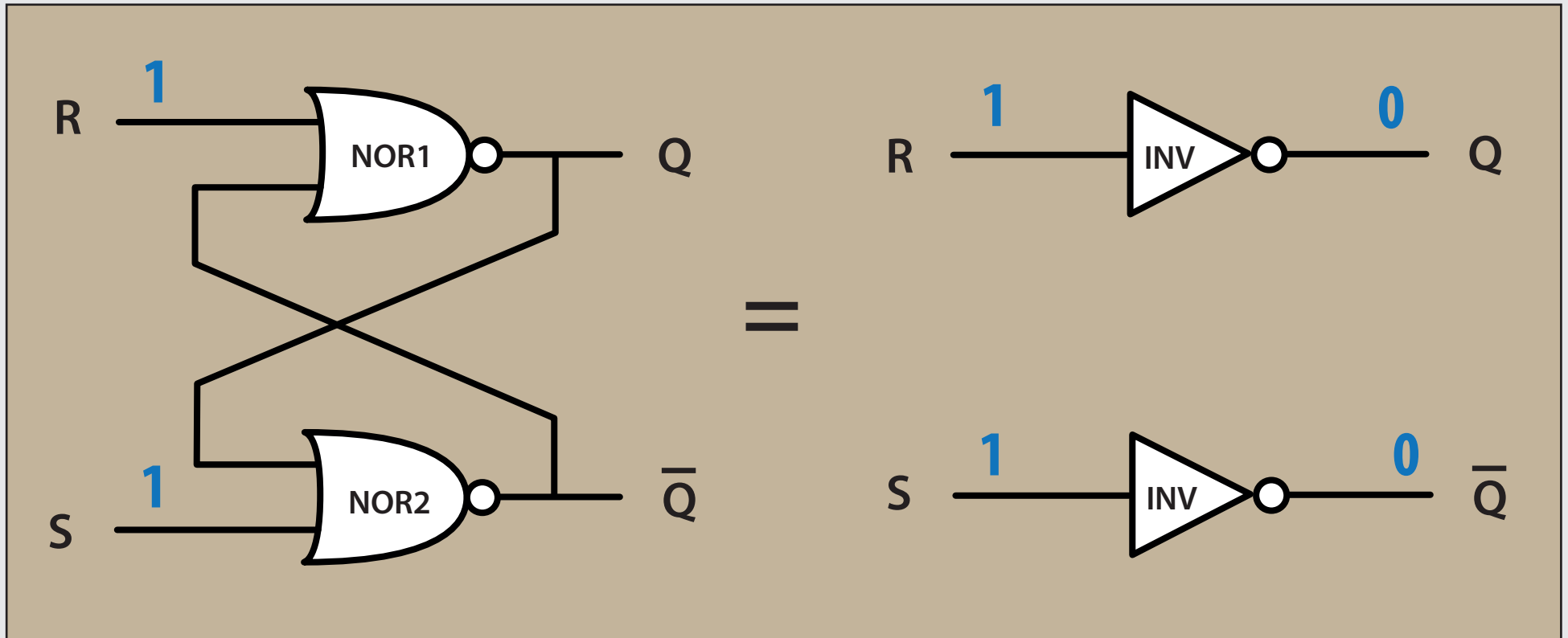


This configuration does not make much sense since :

- Set is designed to set the bit Q to 1
- Reset is designed to reset the bit Q to 0

For that reason, this configuration is generally avoided in real-life situation.

# Application to the SR-latch


Set = 0 & Reset = 0

 

The SR-latch behaves as a pair of cross-coupled inverters and *thus remains in the last encountered stable state.*

# Application to the SR-latch

Set = 0 & Reset = 0

 

The SR-latch behaves as a pair of cross-coupled inverters and *thus remains in the last encountered stable state.*

# The « truth table » with memory of a SR-latch

| S | R | Q              | $\bar{Q}$      |
|---|---|----------------|----------------|
| 0 | 0 | previous state | previous state |
| 0 | 1 | 0              | 1              |
| 1 | 0 | 1              | 0              |
| 1 | 1 | 0              | 0              |


keeps  
memory

reset memory bit  
to zero

set memory bit  
to one

usually avoided  
configuration

# The SR latch symbol

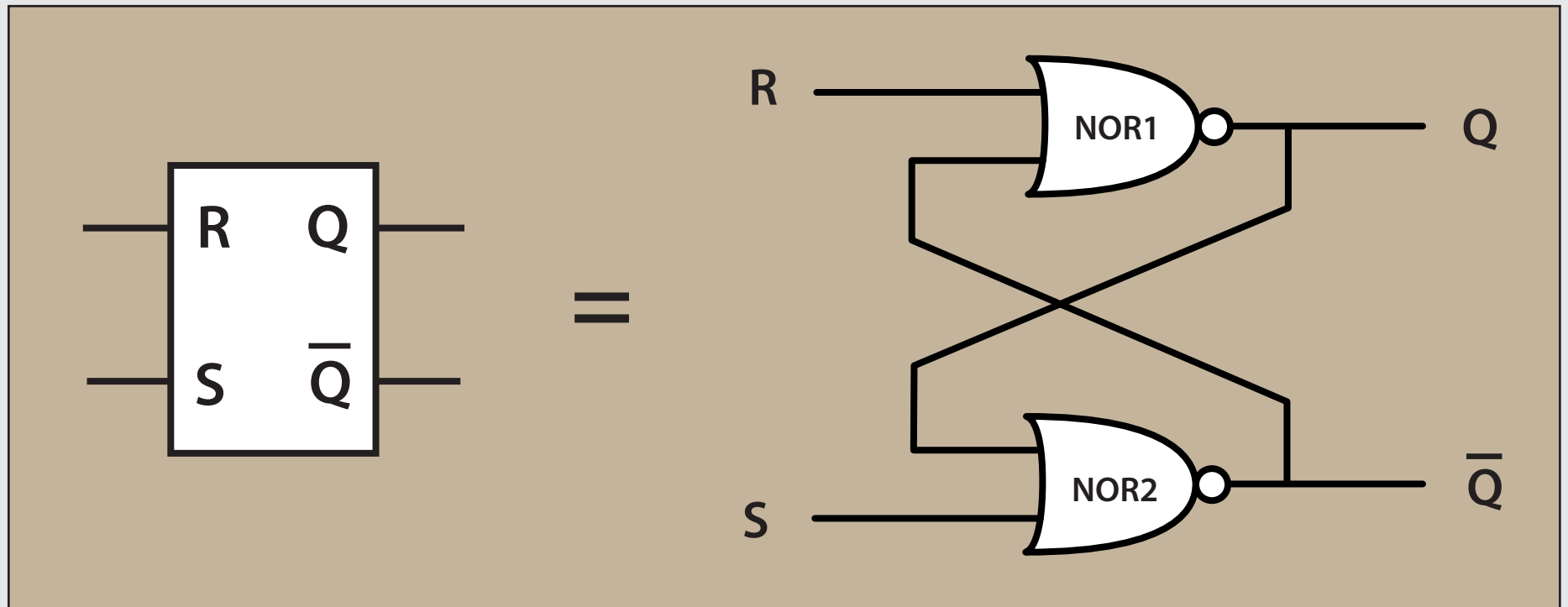

The SR latch is such a basic and fundamental circuit that it has a symbol to represent it.



**D latches  
&&  
D flip-flops**


# D latches

SR latches are awkward for two reasons :


- the behavior when  $S = 1$  and  $R = 1$  is a bit unexpected
- the S and R inputs conflate the issues of « *what* » and « *when* » because asserting one of the inputs determines not only *what* the state should be but also *when* it should change...

In order to solve these problems, the D latch has two inputs :

 - the *data* input **D** controls *what* the next state should be
- the *clock* input **CLK** controls *when* the state should change



 
# Two other useful equalities to remember



# Application to the D latch


CLK = 0

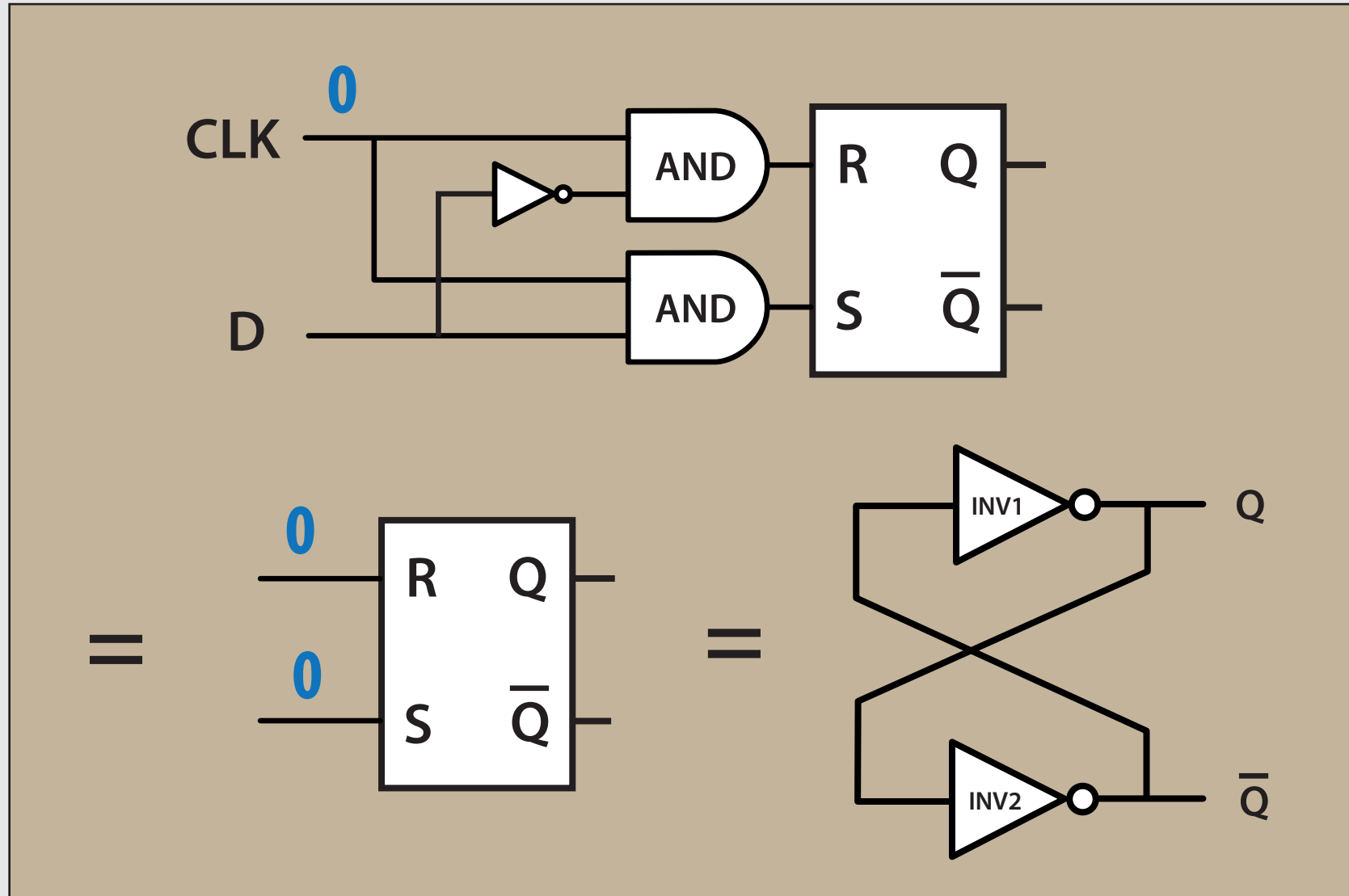

The D latch thus behaves as pair of cross-coupled inverters when CLK = 0  
One says in that case that the D latch is « opaque » since it retains the old value of Q

# Application to the D latch

CLK = 1

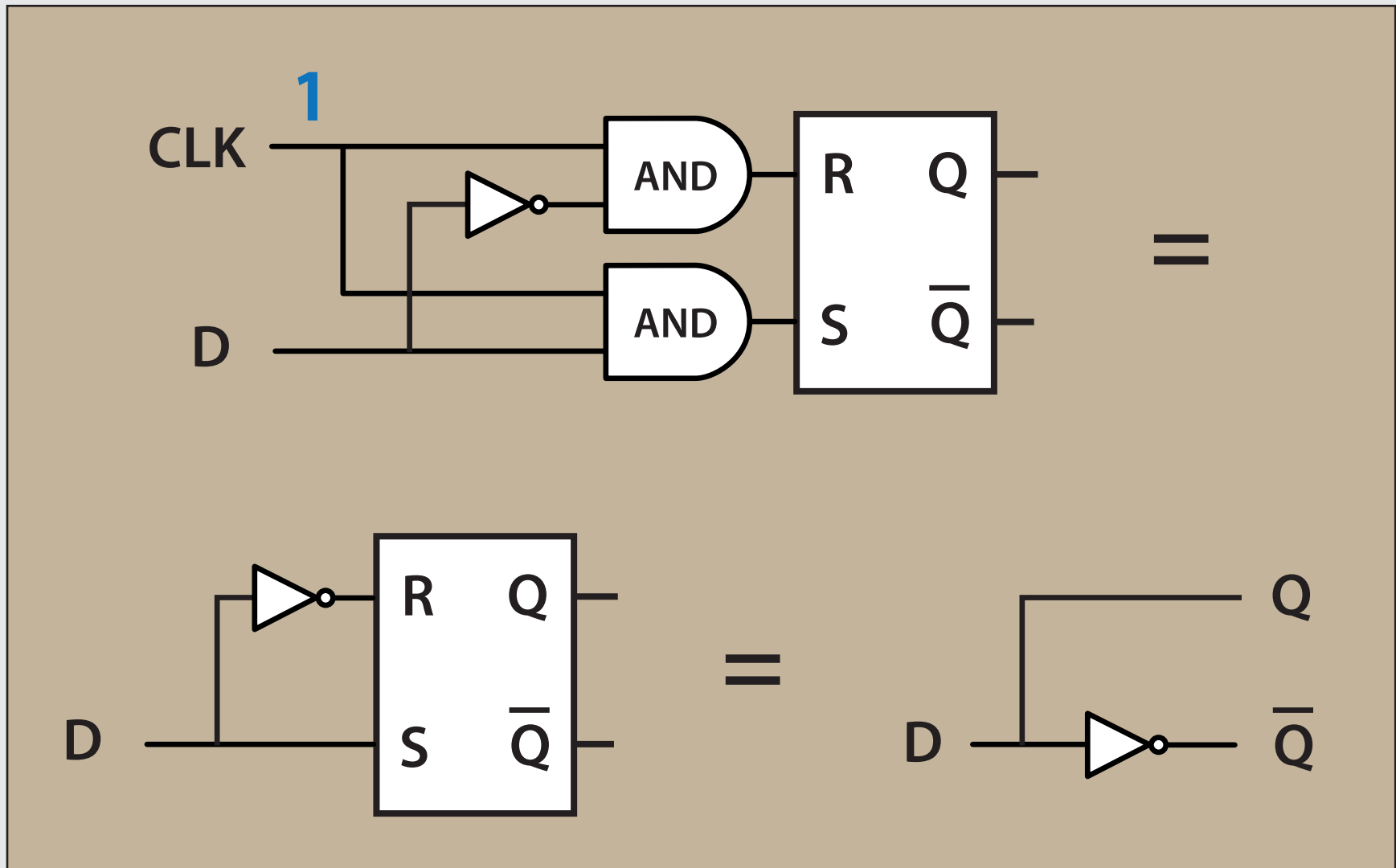


The D latch thus behaves as the « identity » when CLK = 1

One says in that case that the D latch is transparent
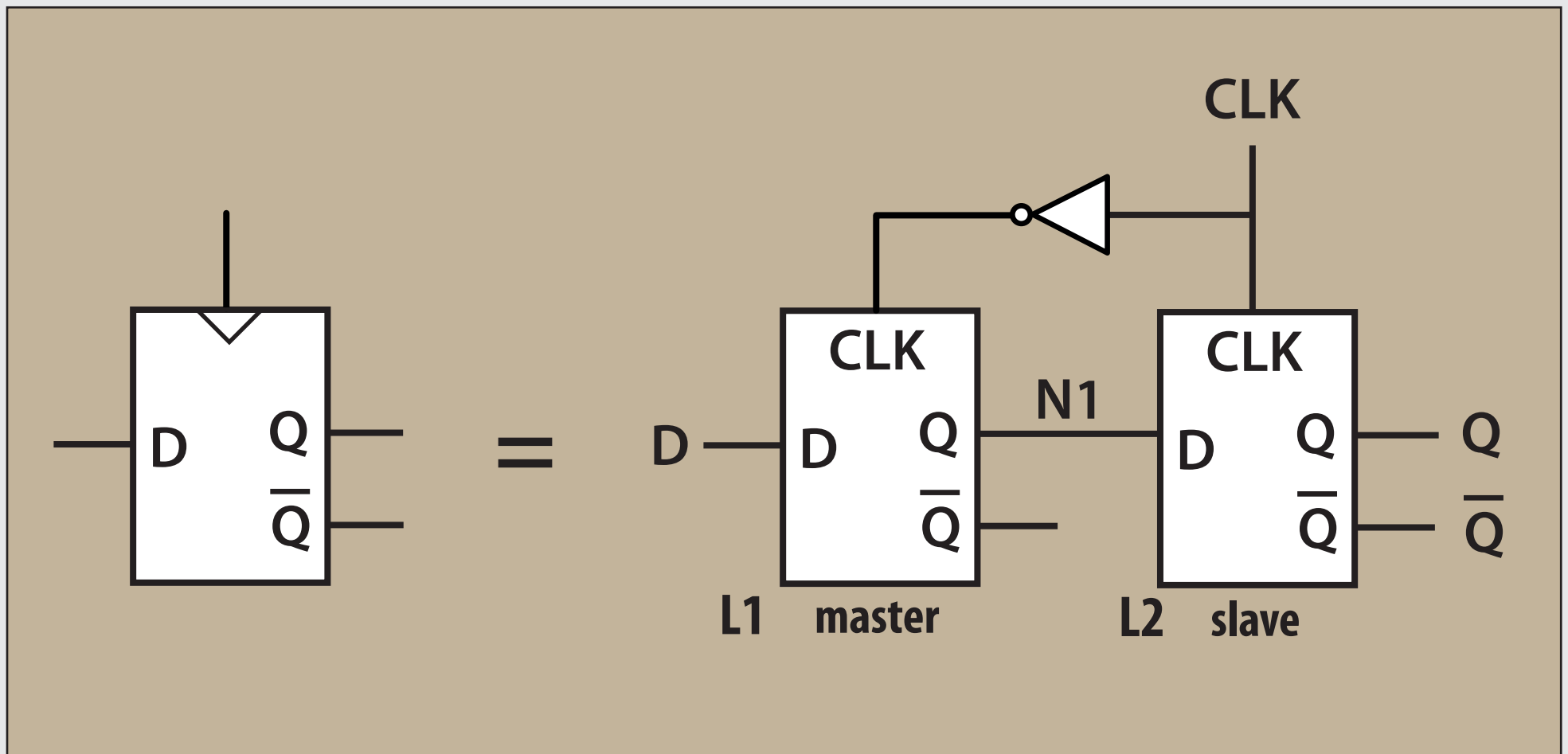
# The D flip-flop

A D flip-flop can be built from two back-to-back D latches controlled by complementary clocks :


- the *master* latch **L1** transparent when  $CLK = 0$
- the *slave* latch **L2** transparent when  $CLK = 1$



# The D flip-flop


A D flip-flop copies **D** to **Q** on the rising edge of the clock and remembers its state at all other times.

On the rising edge of the clock :

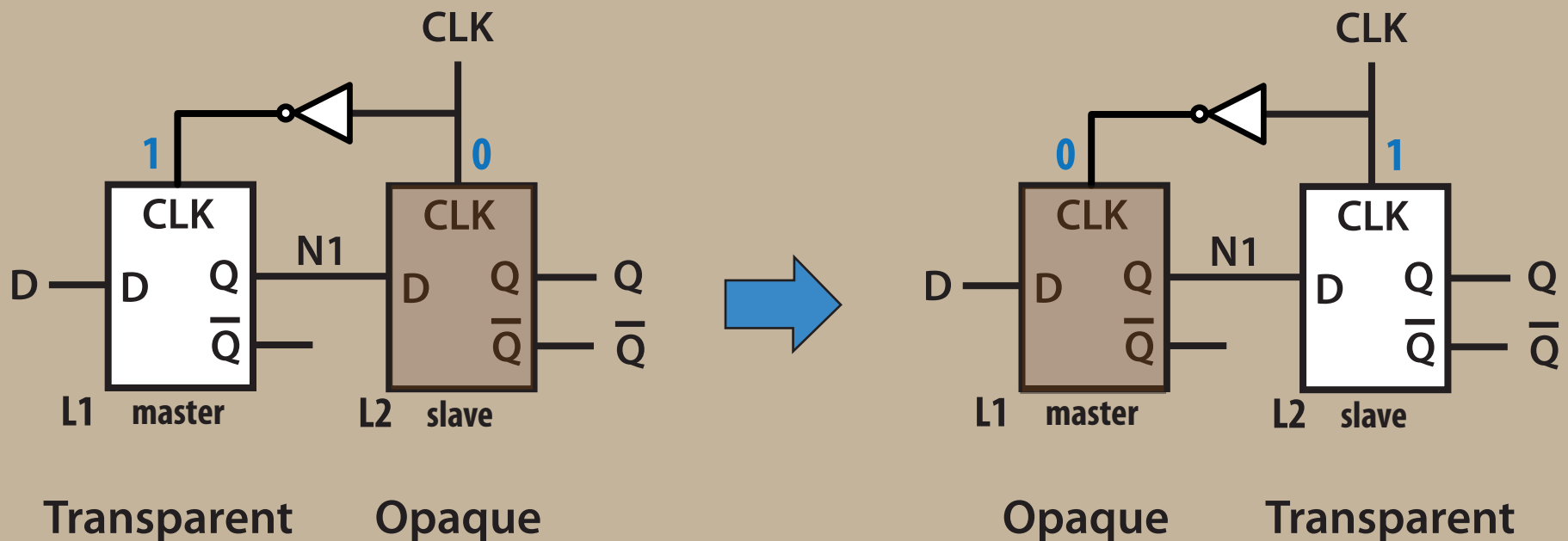


The D flip-flop is also called **master-slave** flip-flop or **positive-edge triggered** flip-flop

# The N-bit Register

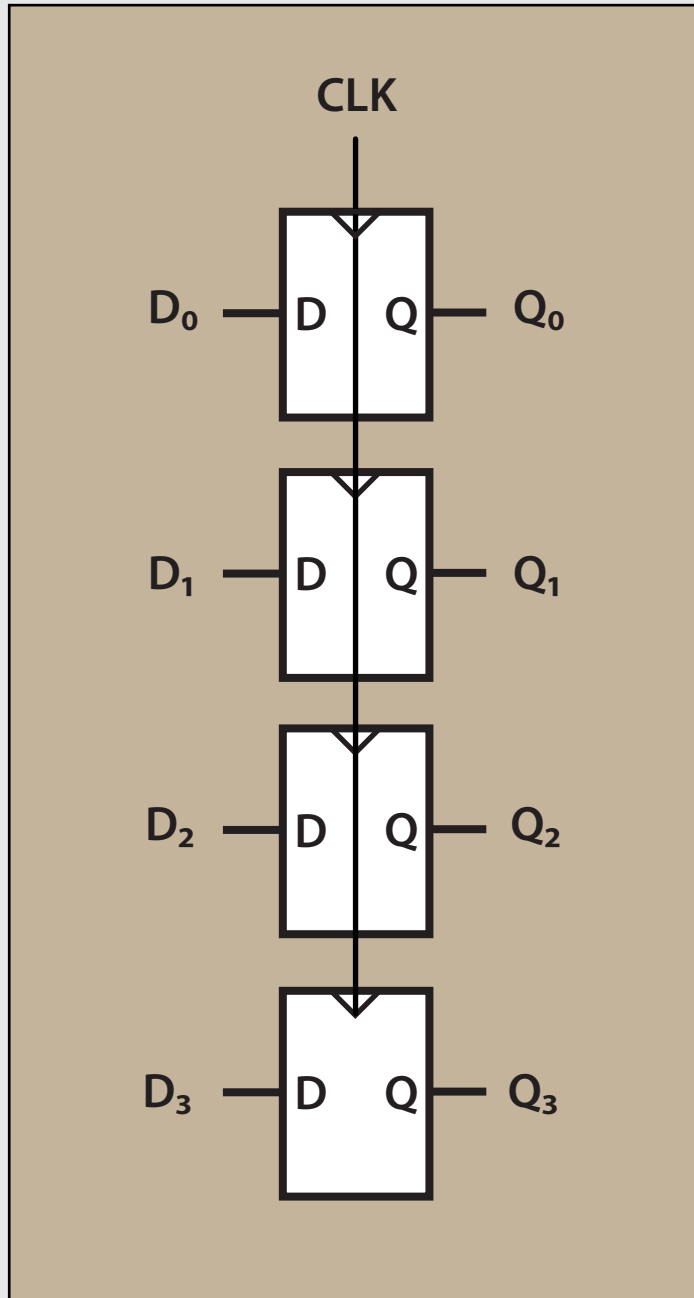

Simply defined as a series of N positive-edge triggered D flip-flops all sharing the same input CLK

## Symbol

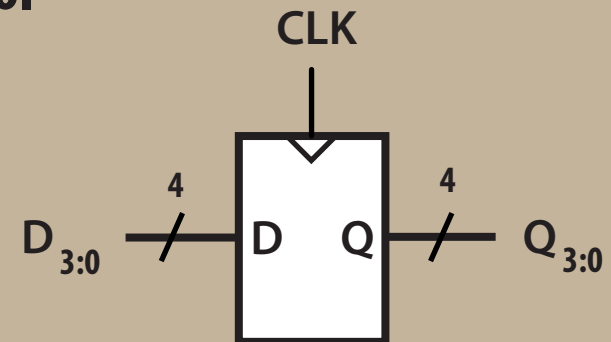




# Exercise 1
 
## H & H Example 3.2


Ben Bitdiddle applies the D and the CLK inputs shown below to a D latch and to a D flip-flop. Help him determine the output Q of each device.



# Solution
 
## H & H Example 3.2

Ben Bitdiddle applies the D and the CLK inputs shown below to a D latch and to a D flip-flop. Help him determine the output Q of each device.




# Sequential Circuits

# Problematic circuits

## 1. astable circuits

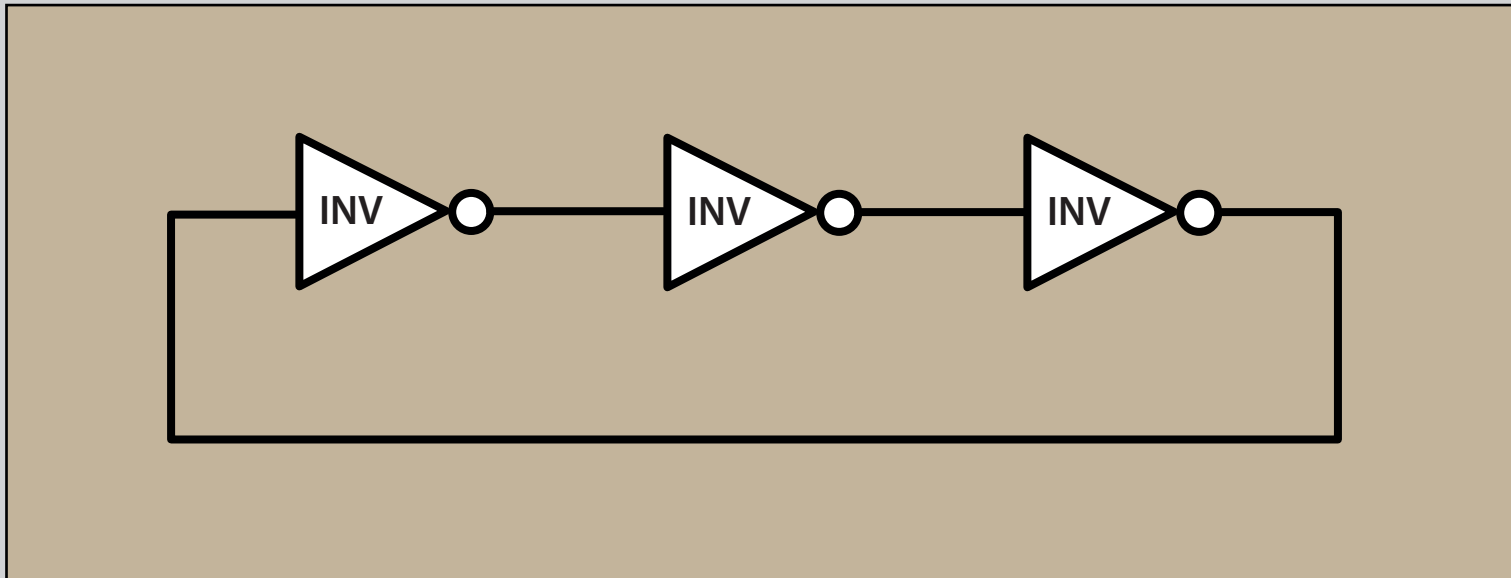
### Exercise :

Suppose that each inverter in the circuit below has delay 1 ns and determine what the circuit does.



 
# Solution

Suppose that each inverter in the circuit below has delay 1 ns and determine what the circuit does.



# Problematic circuits

## 2. race conditions

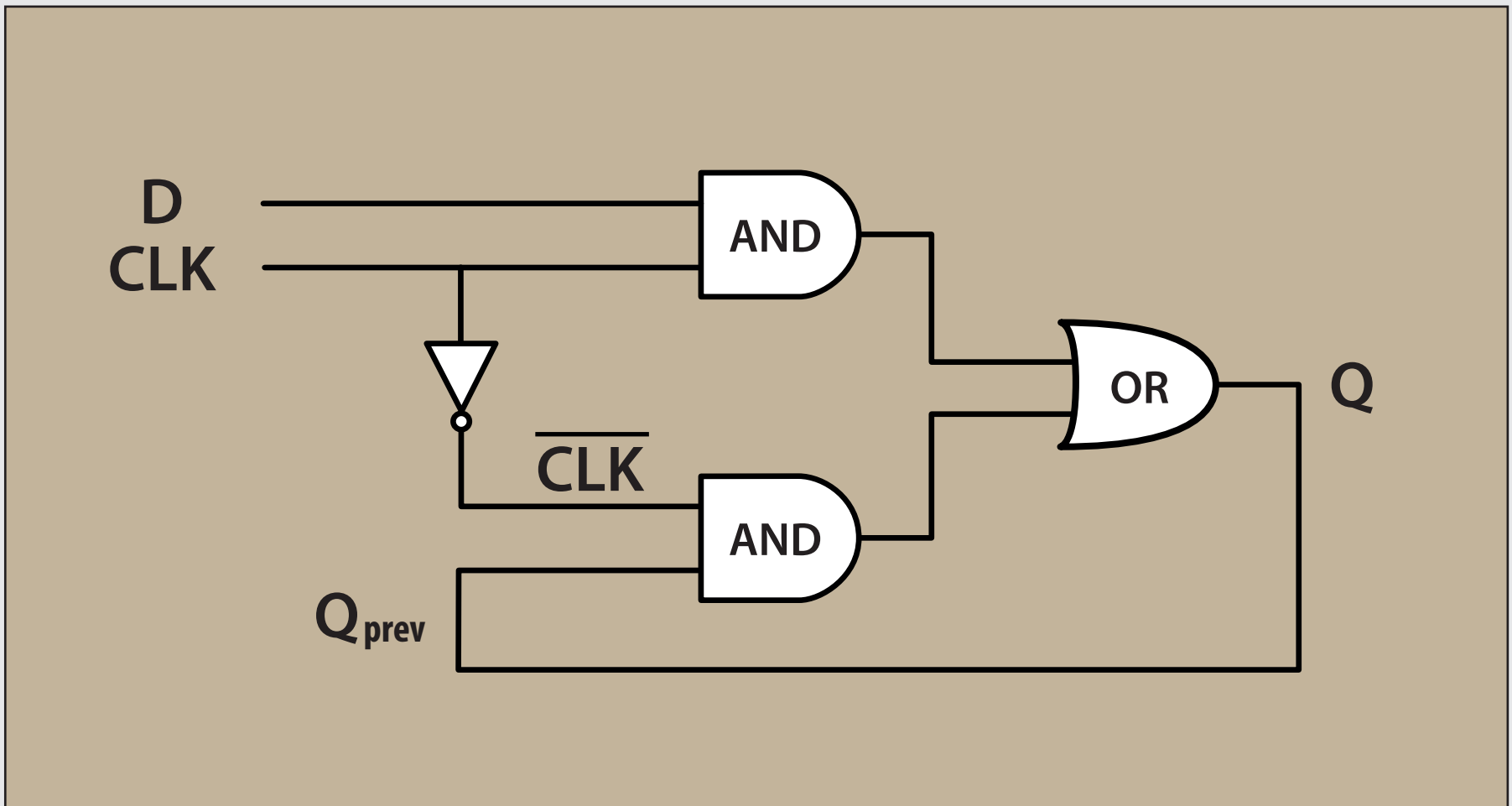


$$Q = \text{CLK} \cdot D + \overline{\text{CLK}} \cdot Q_{\text{prev}}$$

# Problematic circuits


## 2. race conditions

| CLK | D | $Q_{\text{prev}}$ | Q |
|-----|---|-------------------|---|
| 0   | 0 | 0                 | 0 |
| 0   | 0 | 1                 | 1 |
| 0   | 1 | 0                 | 0 |
| 0   | 1 | 1                 | 1 |
| 1   | 0 | 0                 | 0 |
| 1   | 0 | 1                 | 0 |
| 1   | 1 | 0                 | 1 |
| 1   | 1 | 1                 | 1 |

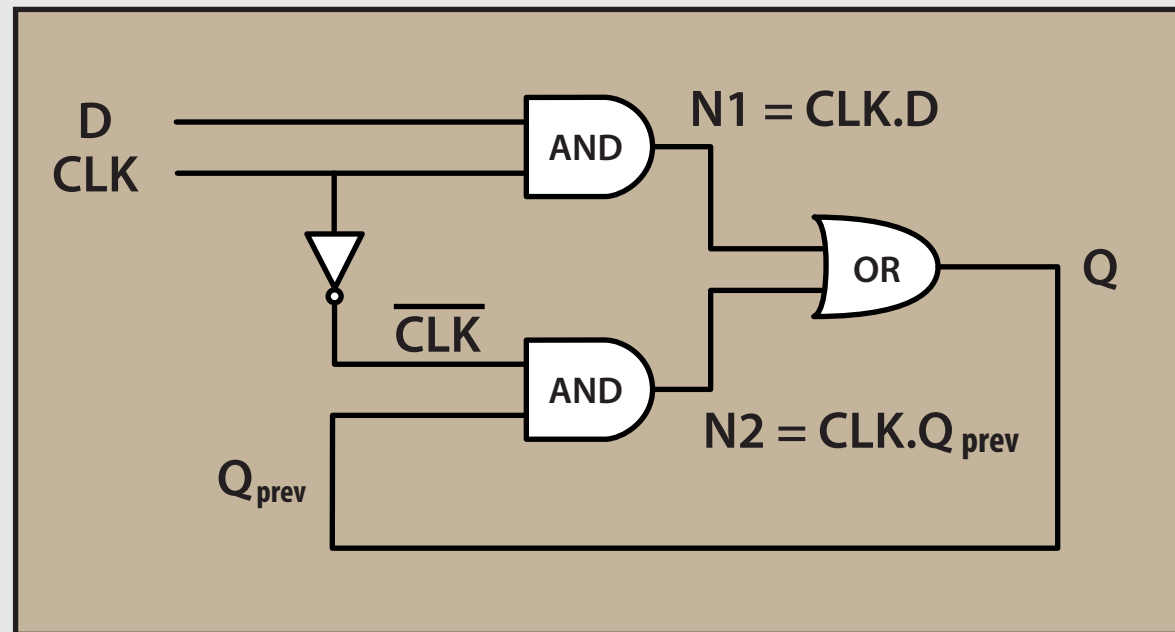

$$Q = \text{CLK} \cdot D + \overline{\text{CLK}} \cdot Q_{\text{prev}}$$

# Race conditions

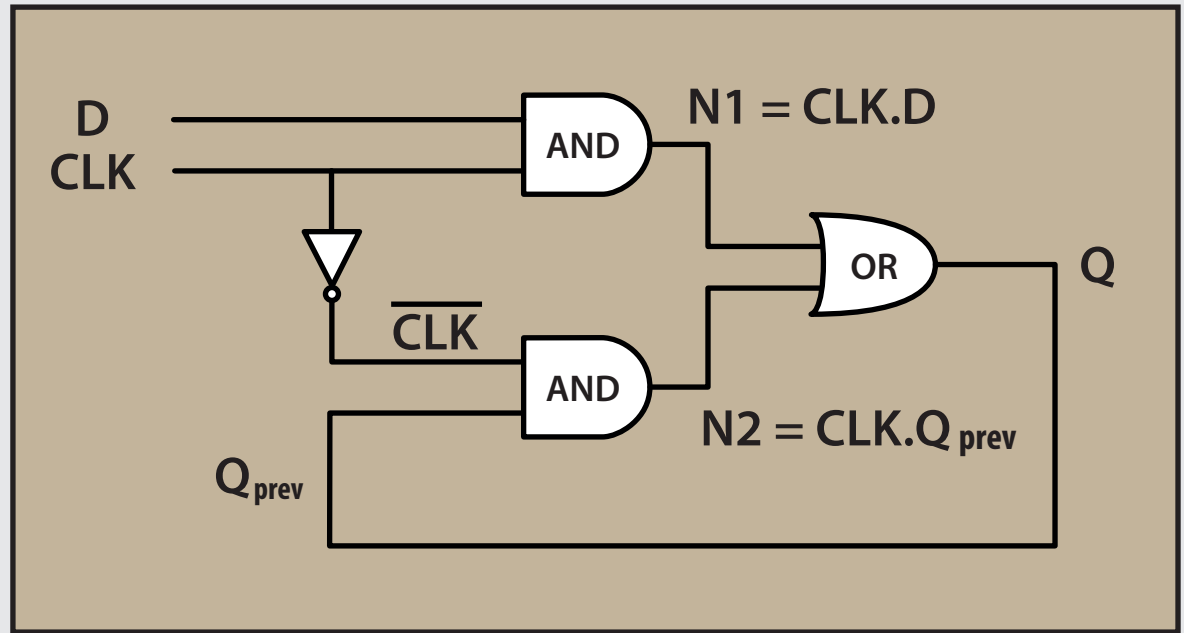


Suppose that  $D = \text{CLK} = 1$

The latch is transparent and thus:  $Q = 1$ .

Now, suppose that CLK falls.

Then, if the delay of the inverter is too long compared to the delays of the AND and OR gates, then  $N1$  and  $Q$  may fall before  $\overline{\text{CLK}}$  rises.

 In that case,  $N2$  will never rise and  $Q$  becomes stuck to 0





# **Synchronous Sequential Circuits**

# Synchronous Sequential Circuits

A circuit is *sequential synchronous* when :

- every circuit element is either a register or a combinational circuit
- at least one circuit element is a register
- all registers receive the same clock signal
- every cyclic path contains at least one register.

Sequential circuits that are not synchronous are called asynchronous.

# Exercise

Which circuits below are *sequential synchronous* ?

