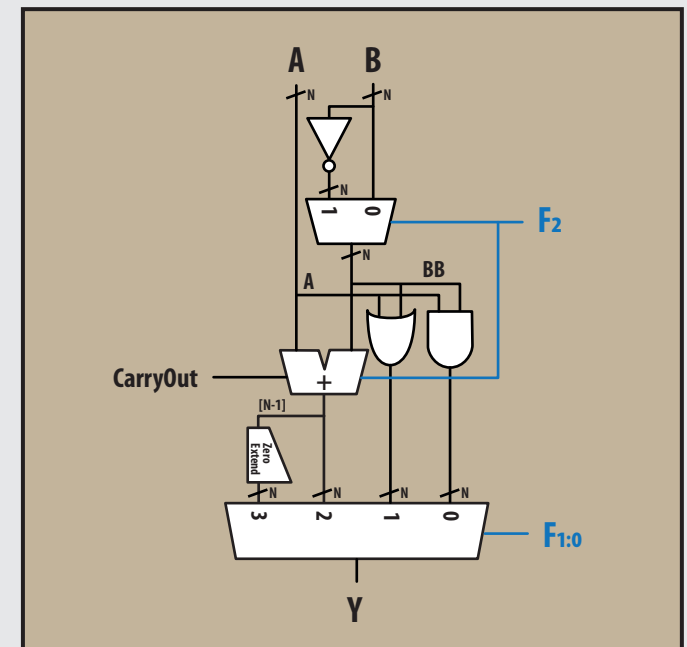


Computer Architecture


Paul Mellies

Lecture 12 : Digital Building Blocks




Arithmetic Circuits

Carry Propagate Adder

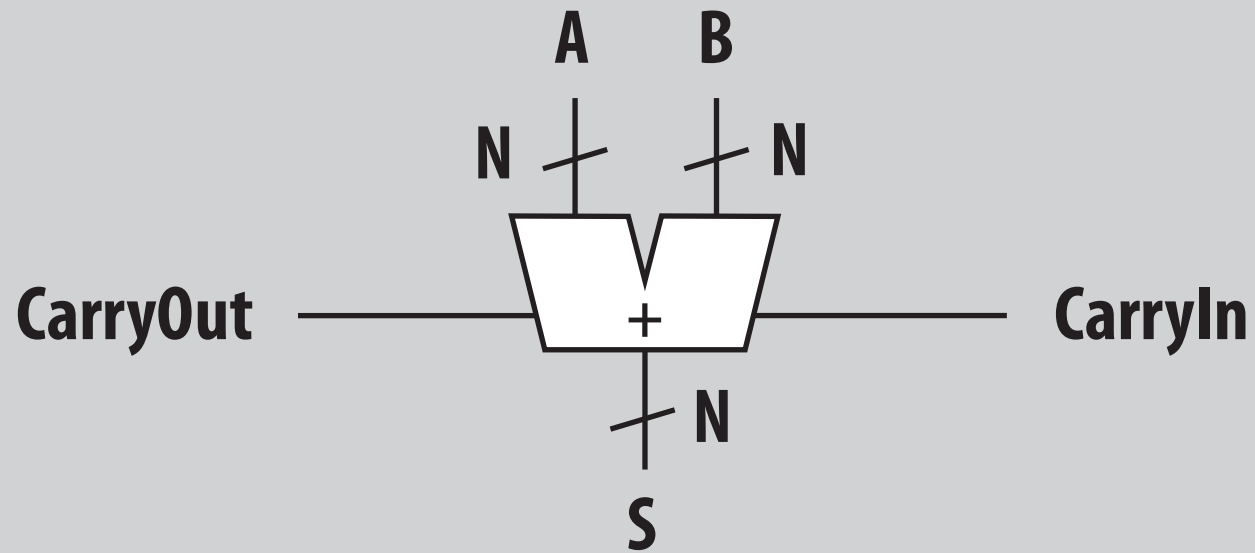

Carry Propagate Adder


Full Adder

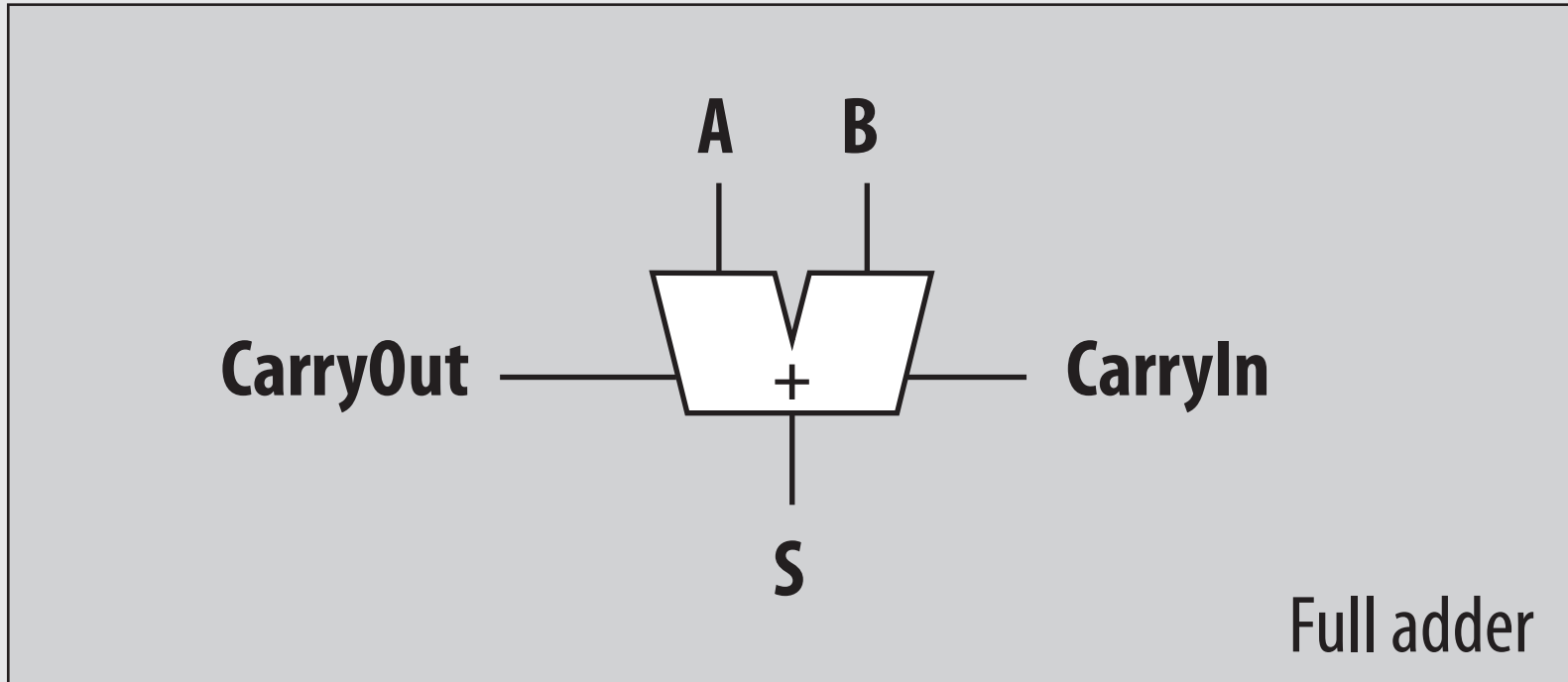

$$S = A \oplus B \oplus \text{CarryIn}$$


$$\text{CarryOut} = A.B + A.\text{CarryIn} + B.\text{CarryIn}$$

Ripple Carry Adder

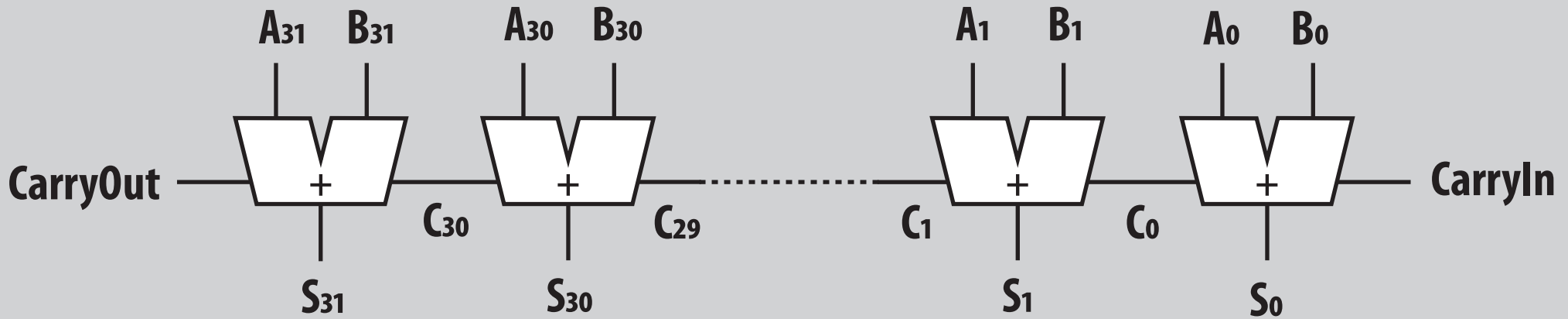


32-bit ripple carry adder

Carry Lookahead Adder

 


32-bit carry lookahead adder

4-bit CLA Block

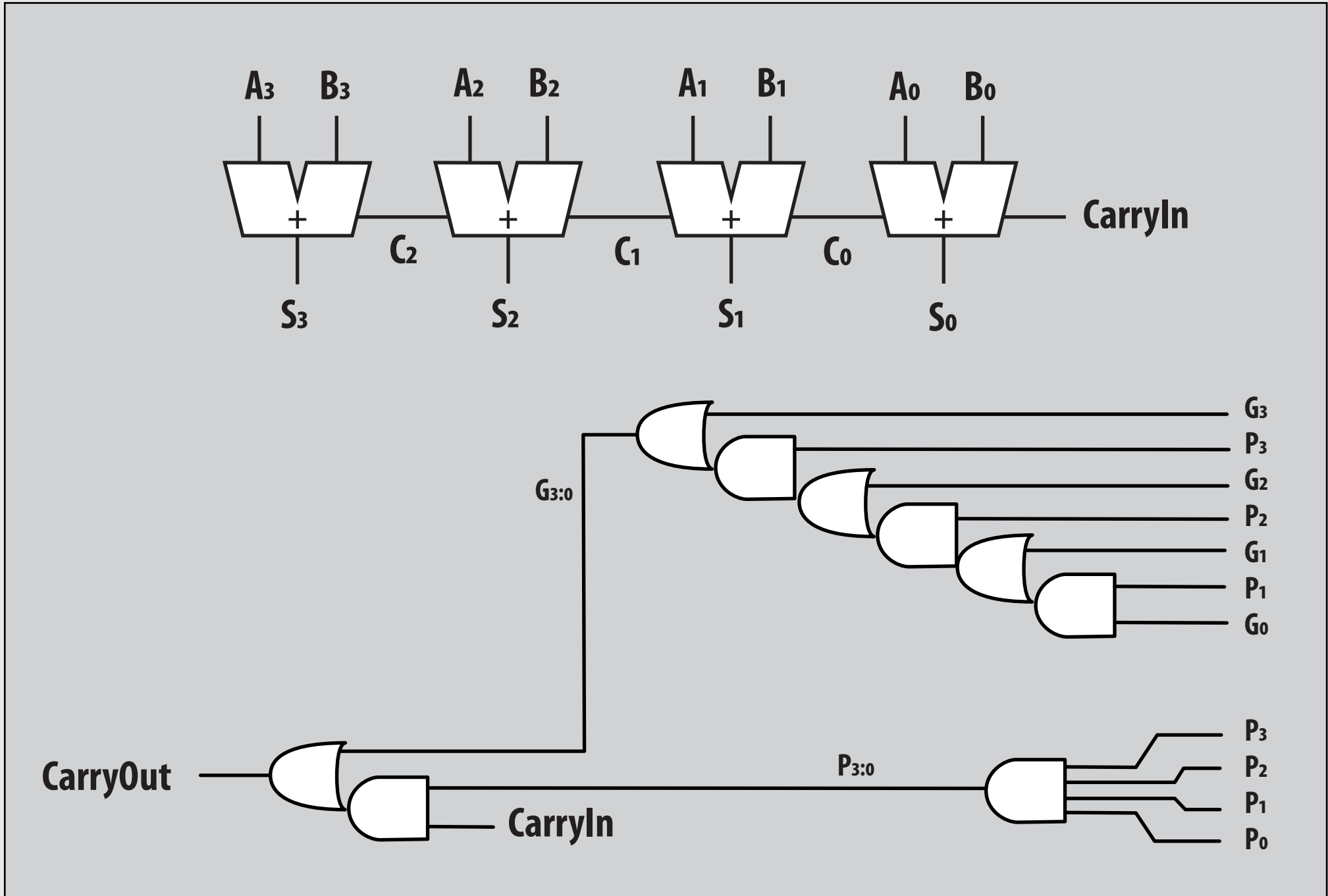

Generate (G) and Propagate (P) signals

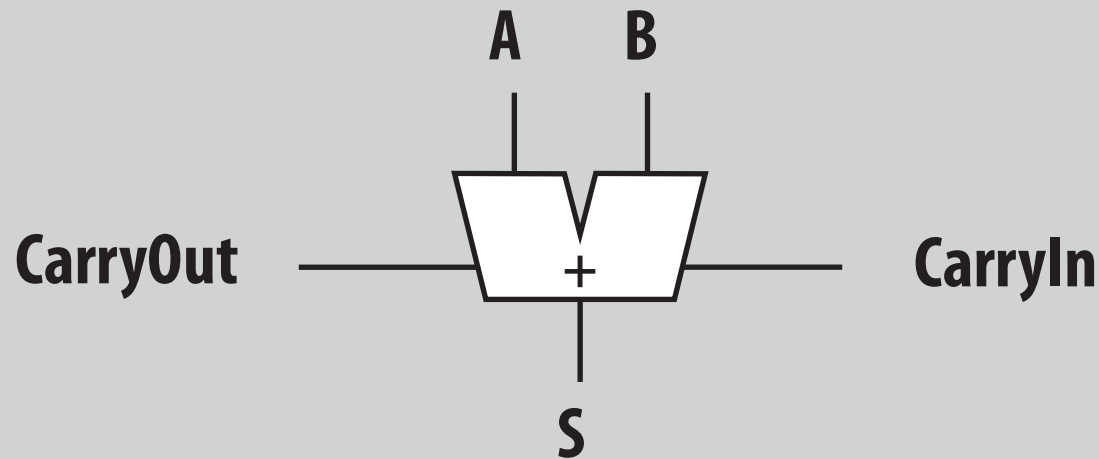

$$\mathbf{G = A \cdot B}$$


$$\mathbf{P = A + B}$$

G = 1 when the adder *generates* a CarryOut whatever the value of CarryIn


P = 1 when the adder *propagates* the CarryIn to the CarryOut

Critical path of the Carry Lookahead Adder

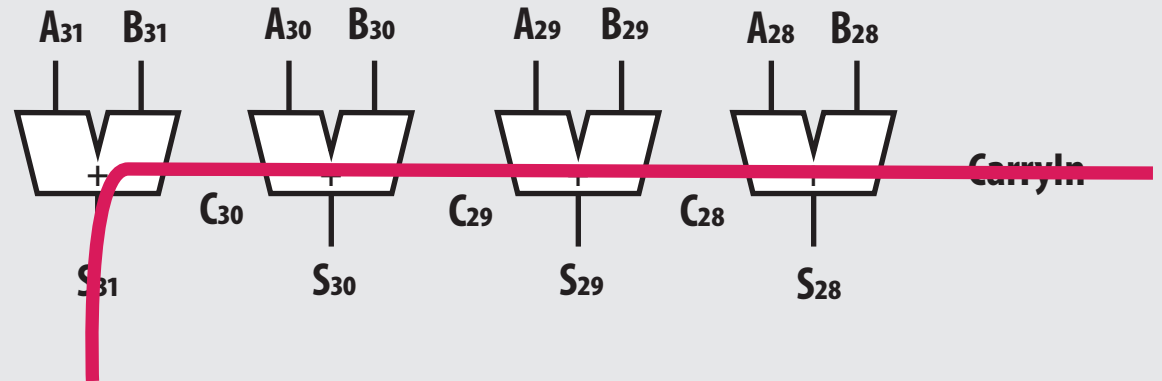
On the lefthand side 4-bit CLA block :
(most significant bits from S_{31} to S_{28})



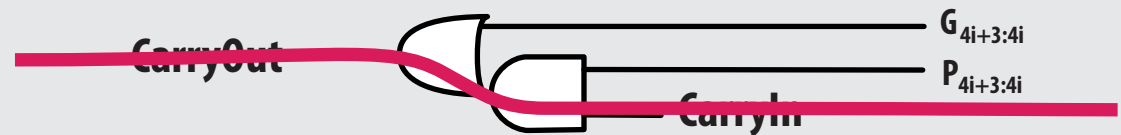On the six internal 4-bit CLA blocks :
 $i = 6, 5, 4, 3, 2, 1$



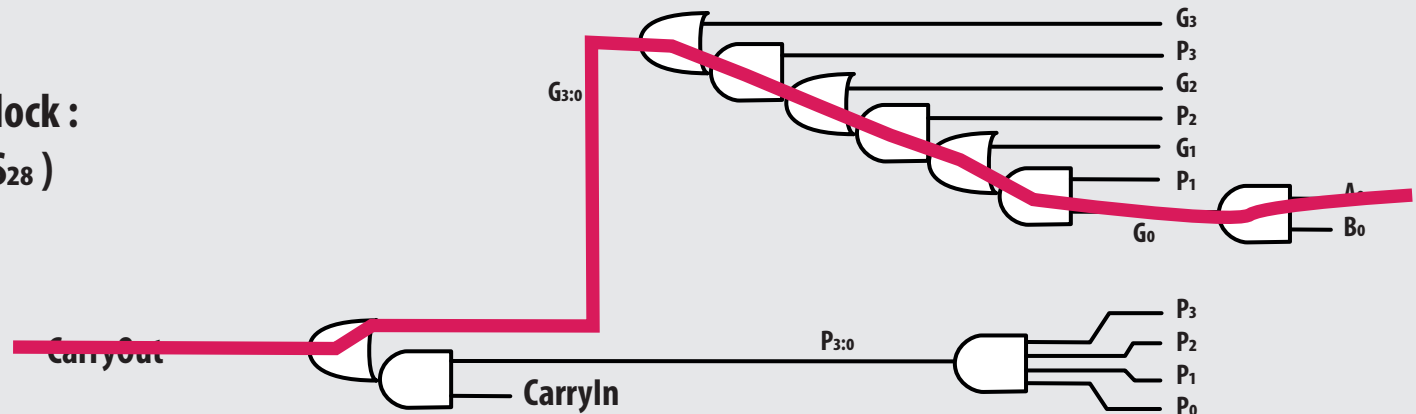On the righthand side 4-bit CLA block :
(less significant bits from S_{31} to S_{28})



Propagation Delay




$$4 t_{\text{FULL_ADDER}}$$

+

$$6 \times (t_{\text{AND}} + t_{\text{OR}})$$

+

$$4 t_{\text{AND}} + 4 t_{\text{OR}}$$

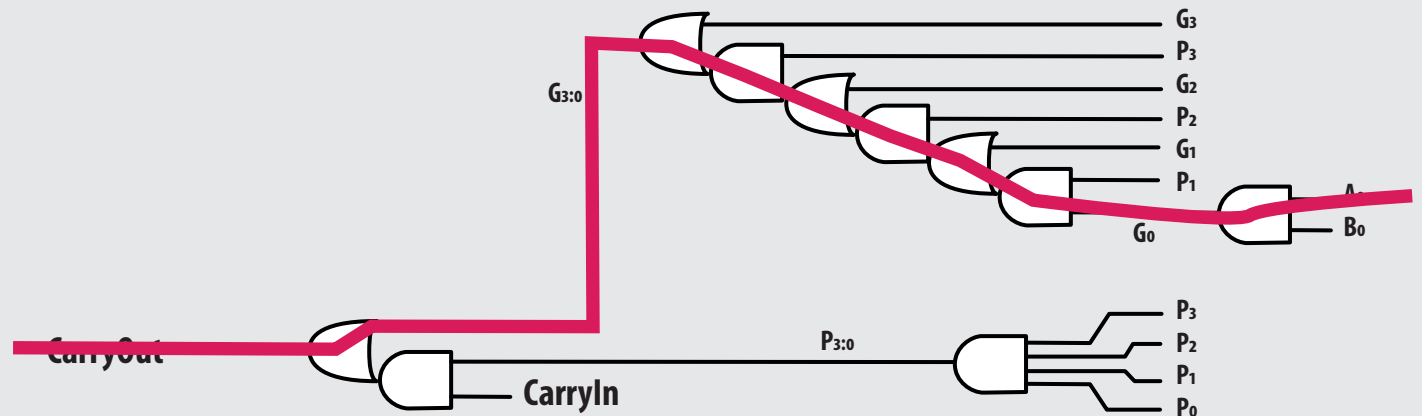 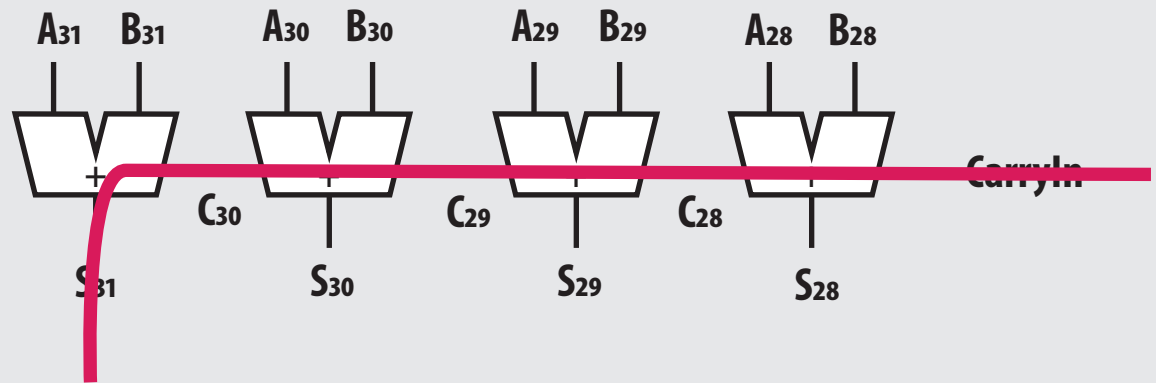

$$t_{\text{CLA}} = 10 t_{\text{AND}} + 10 t_{\text{OR}} + 4 t_{\text{FULL_ADDER}}$$

Exercise

(H&H Example 5.1)

Compare the delays of a 32-bit ripple-carry adder and a 32-bit carry-lookahead adder with 4-bit blocks.

Assume that each two-input gate delay is 100 ps and that a full adder delay is 300 ps.

Solution

(H&H Example 5.1)

Compare the delays of a 32-bit ripple-carry adder and a 32-bit carry-lookahead adder with 4-bit blocks.

Assume that each two-input gate delay is 100 ps and that a full adder delay is 300 ps.

32-bit ripple-carry adder:

$$32 \times 300 \text{ ps} = 9\,600 \text{ ps} = 9.6 \text{ ns}$$

32-bit carry-lookahead adder:



$$10 \times 100 \text{ ps} + 10 \times 100 \text{ ps} + 4 \times 300 \text{ ps} = 3\,200 \text{ ps} = 3.2 \text{ ns}$$

Carry Lookahead Adder (summary)


The 32-bit Carry Lookahead Adder is faster than the 32-bit Ripple Carry Adder because :

1. In each 4-bit block, the generate and propagate signals do not depend on the input signal **CarryIn**.
2. for that reason, the two signals can be computed *independently* and *in parallel* by each 4-bit block.
3. once a 4-bit block « knows » the values of the two signals **P** and **G**, it can generate and/or transmit carries much faster.
4. for that reason, each 4-bit block « receives » the signal **CarryIn** faster than in the Ripple Carry Adder circuit.



Subtraction

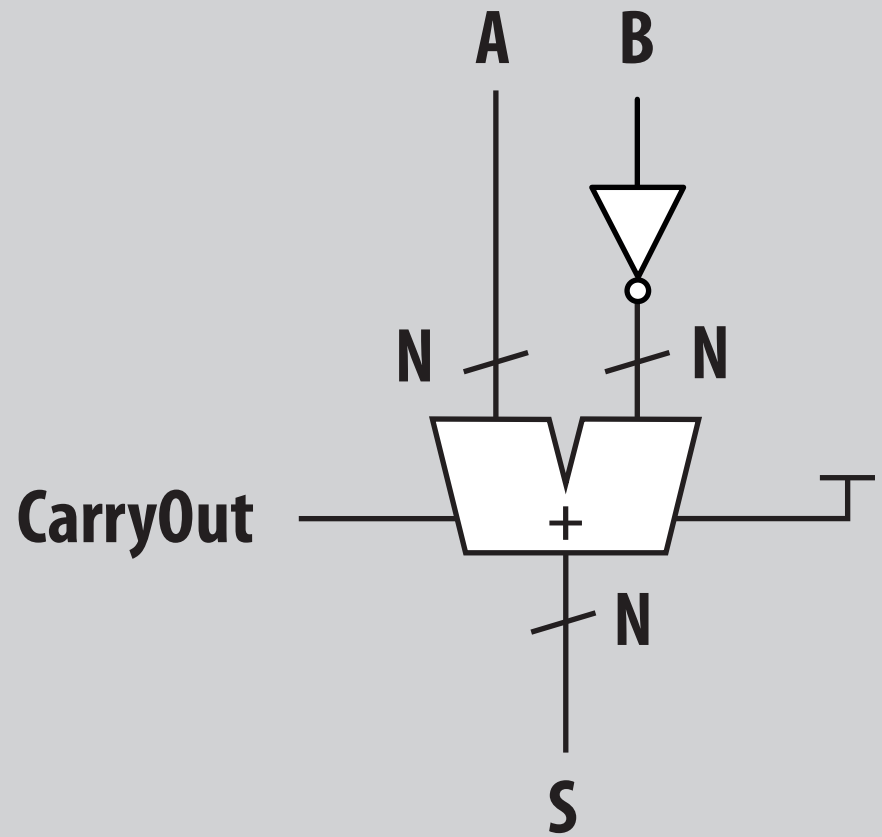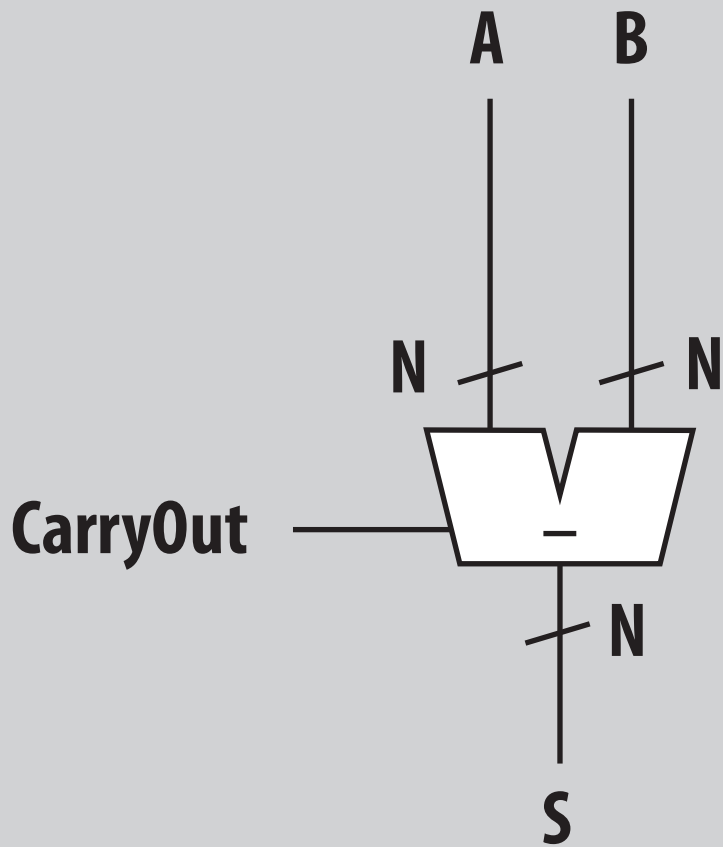

Equality Operator

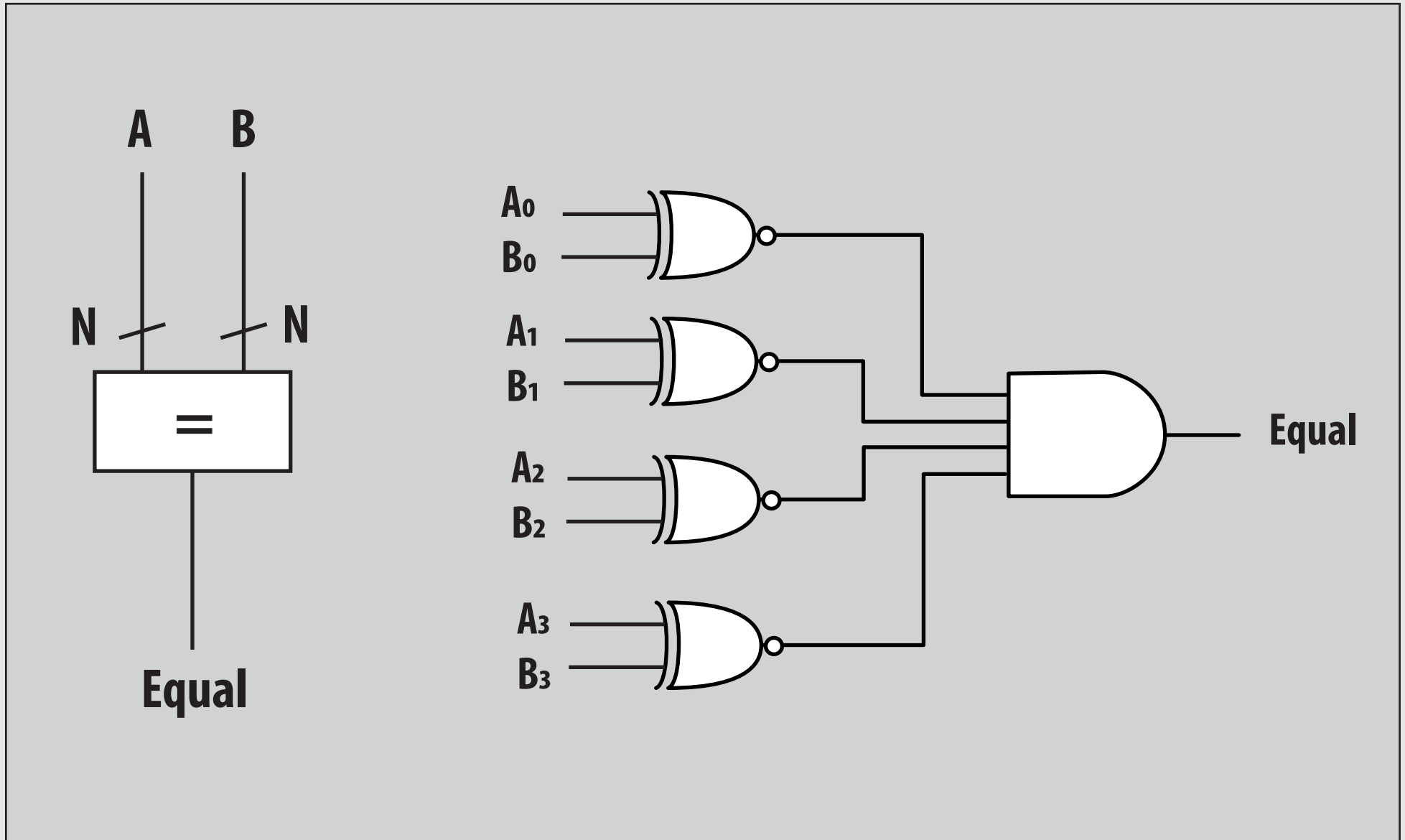


Magnitude Operator

  


Arithmetic Logical Unit (ALU)

F_{2:0}	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT


 


Arithmetic Logical Unit (ALU)



$F_{2:0}$	Function
000	A AND B
001	A OR B
010	A + B
011	not used
100	A AND \bar{B}
101	A OR \bar{B}
110	A - B
111	SLT

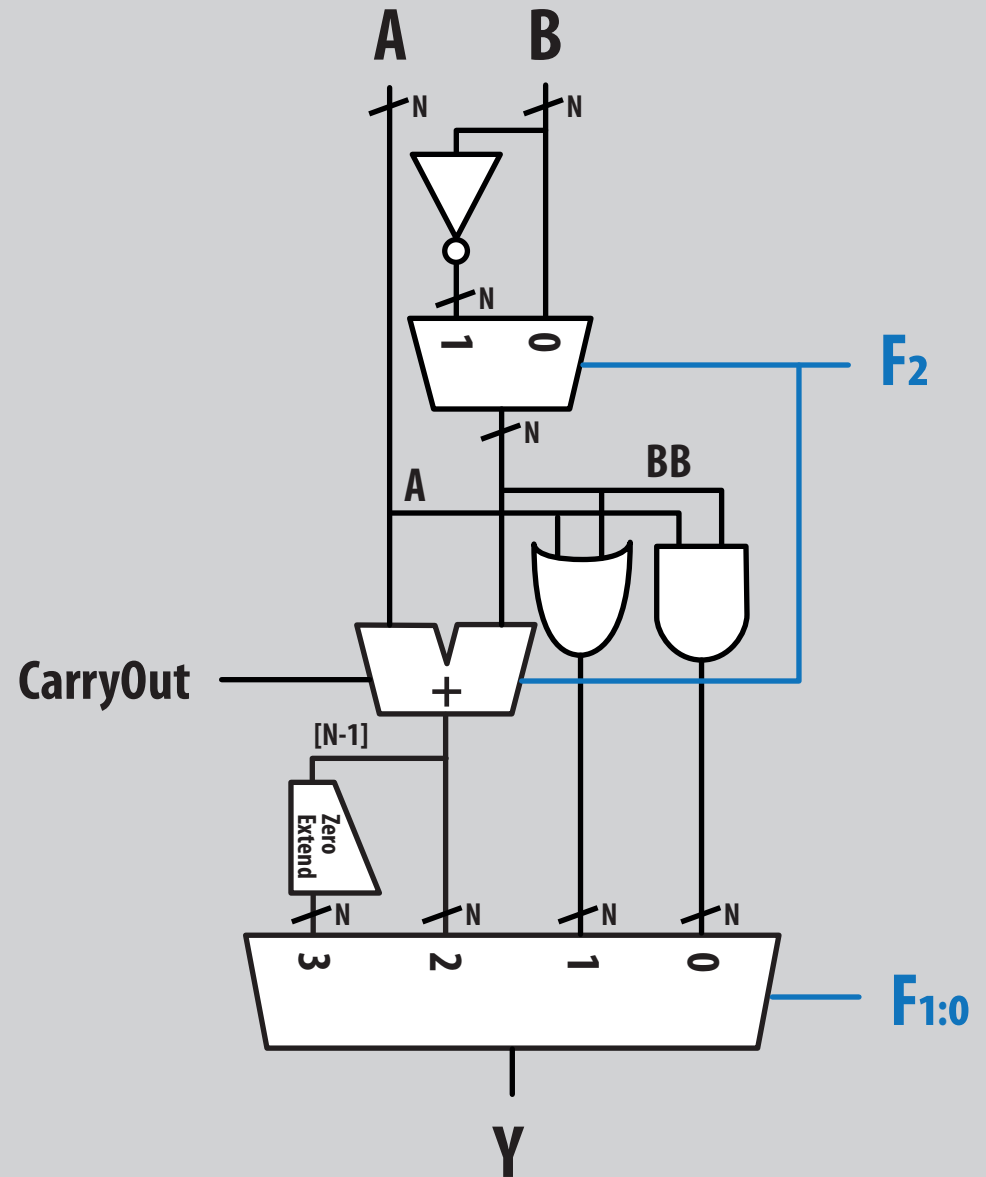



Shift Left

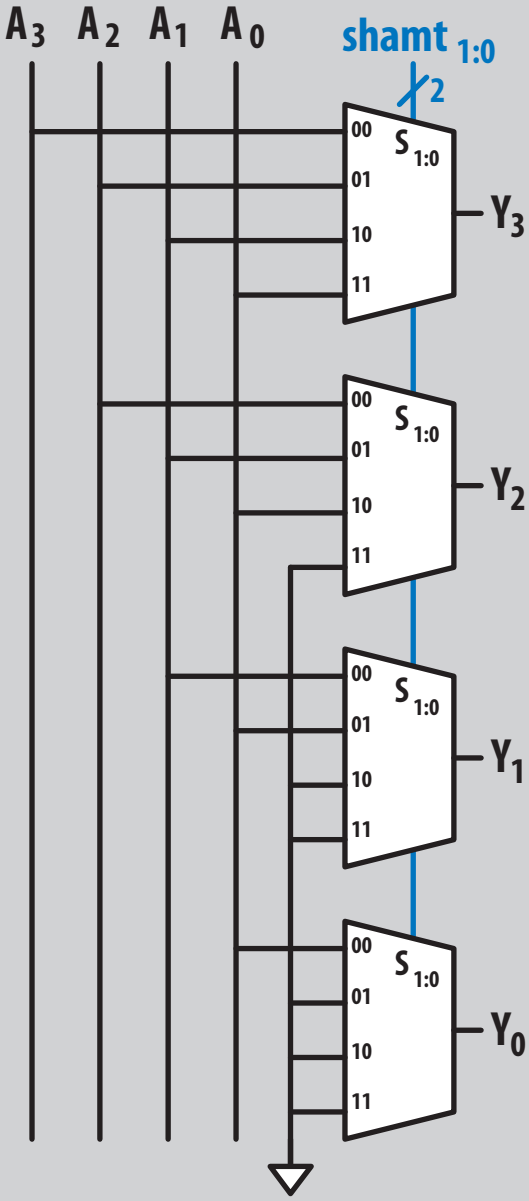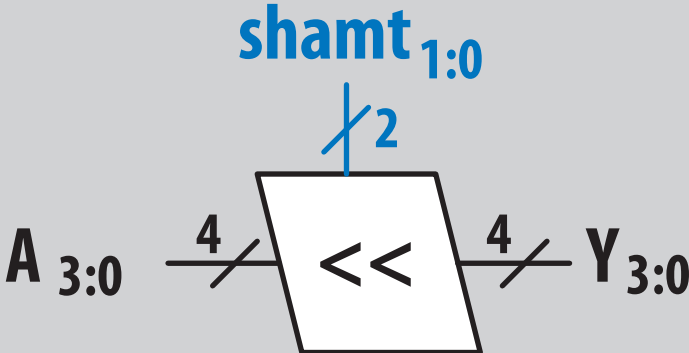

Shift Right

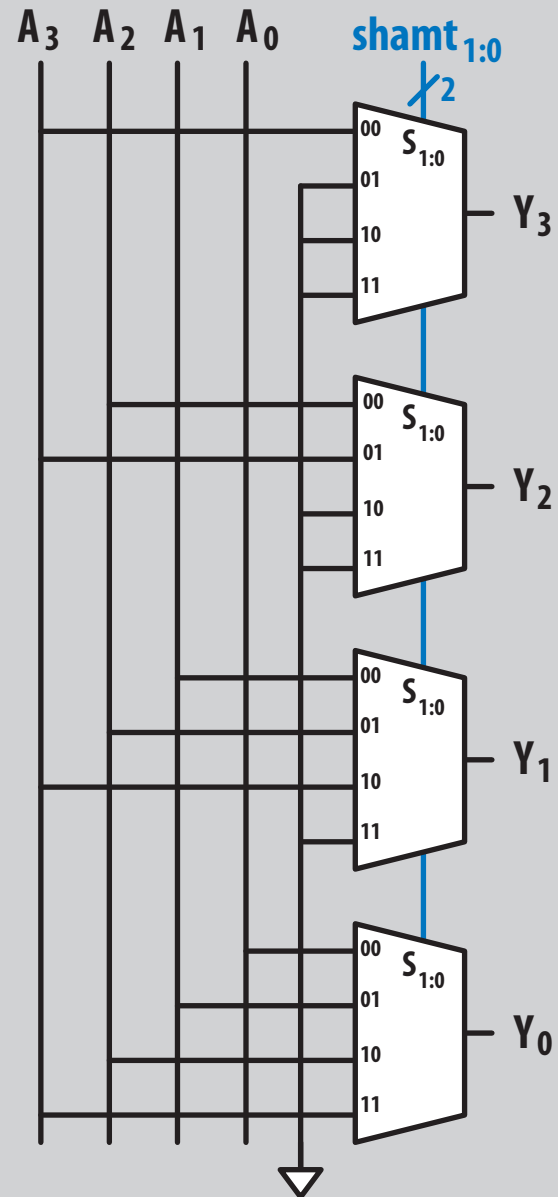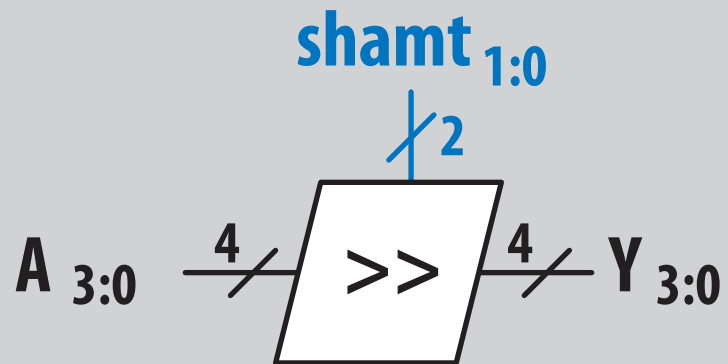

Arithmetic Shift Right

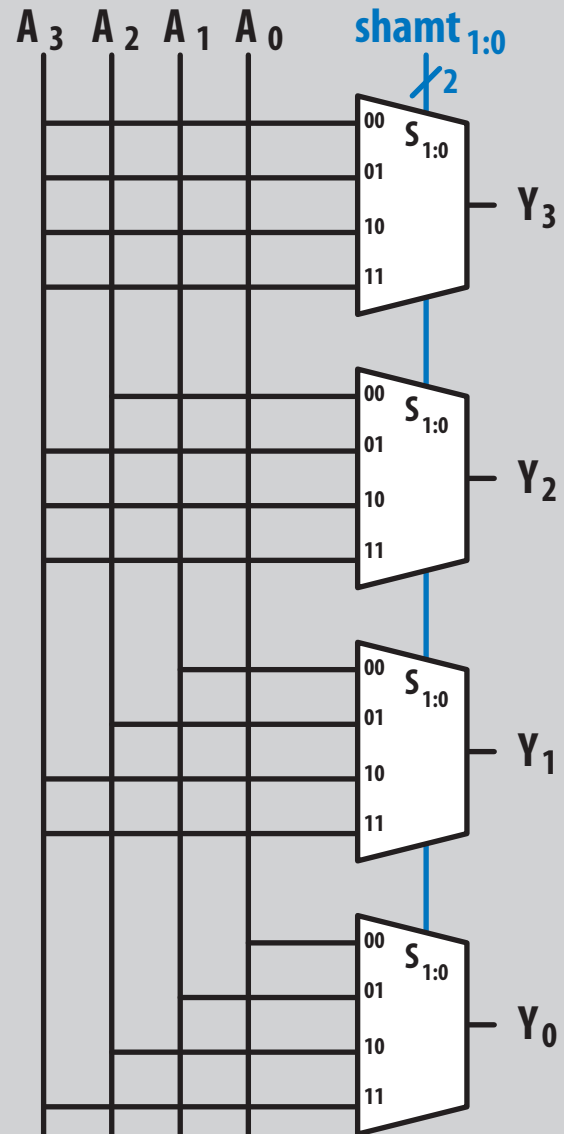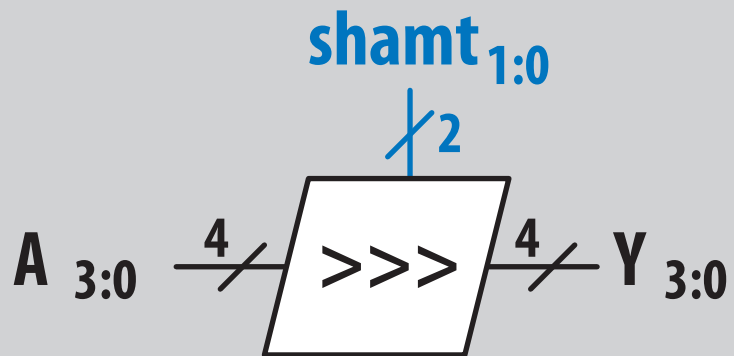

Multiplication

Multiplication

				A_3	A_2	A_1	A_0	
			\times	B_3	B_2	B_1	B_0	
				A_3B_0	A_2B_0	A_1B_0	A_0B_0	
			A_3B_1	A_2B_1	A_1B_1	A_0B_1		
		A_3B_2	A_2B_2	A_1B_2	A_0B_2			
$+$	A_3B_3	A_2B_3	A_1B_3	A_0B_3				
	P_7	P_6	P_5	P_4	P_3	P_2	P_1	P_0

The multiplication algorithm performed sequentially


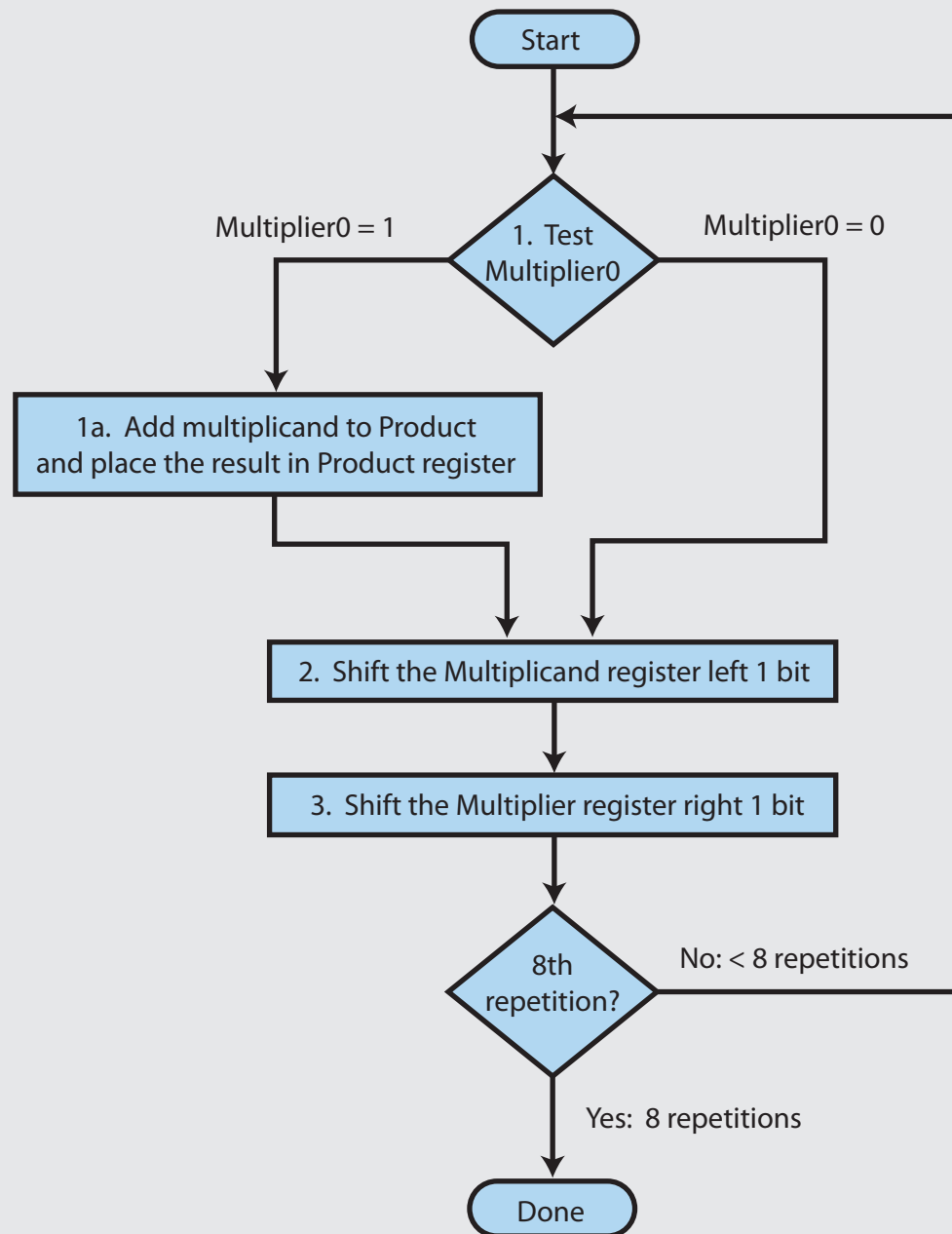


Figure 3.4 in
Patterson and Hennessy

Multiplication

 

Division

Division Algorithm $A \div B$ for N-bit unsigned numbers

```
R' = 0
for i = N-1 to 0
  R = { R' << 1, Ai } // shift R' to the left
                        // with Ai as least significant bit

  D = R - B
  if D < 0 then Qi = 0, R' = R // R < B
  else          Qi = 1, R' = D // R >= B
R = R'
```

The partial remainder R is initialized to 0

The most significant bit of the dividend A becomes the least significant bit of R

The divisor B is repeatedly subtracted from this partial remainder to determine whether it fits :

- if the difference $R - B$ is negative, then the quotient bit Q_i is 0 and the difference is discarded.
- if the difference $R - B$ is positive, then the quotient bit Q_i is 1 and the partial remainder is updated to be the difference $R - B$.




Exercise :

Use the algorithm to compute $A \div B$ for :

1. $A = 83$ and $B = 5$
2. $A = 97$ and $B = 23$




```
R' = 0
for i = N-1 to 0
  R = { R' << 1 , Ai } // shift R' to the left
                        // with Ai as least significant bit
  D = R - B
  if D < 0 then Qi = 0 , R' = R // R < B
  else          Qi = 1 , R' = D // R >= B
R = R'
```

Array Divider

   


Exercise :

Explain how the circuit works !

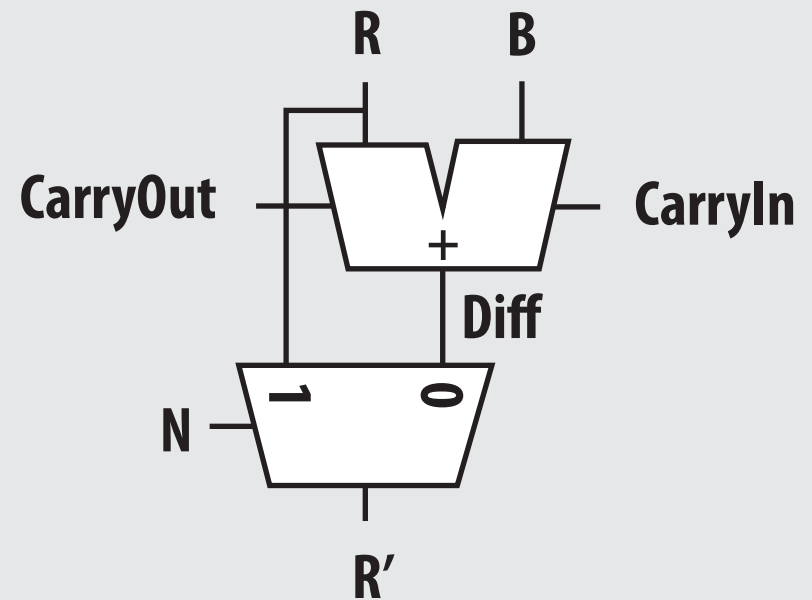 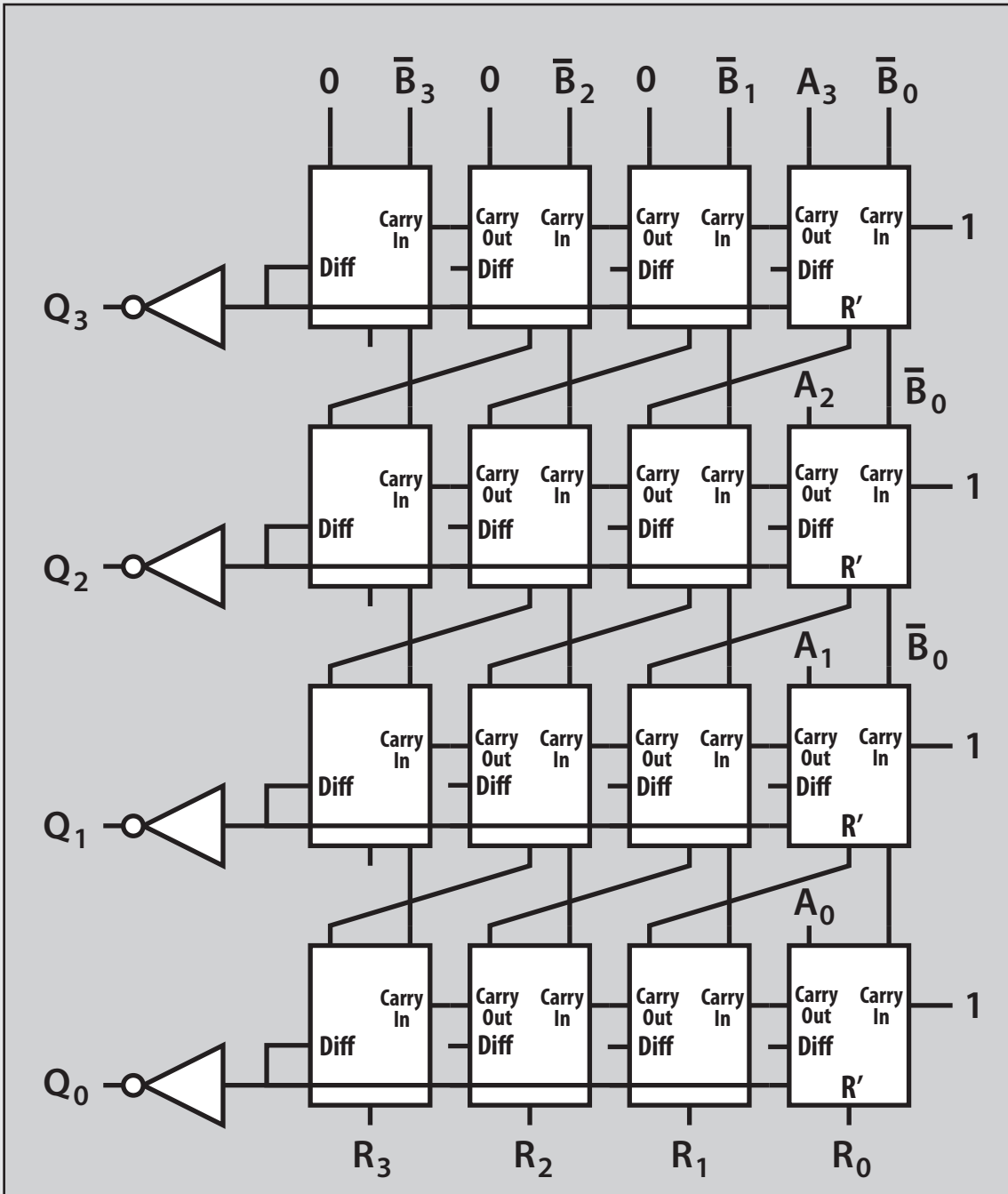


Sequential Building Blocks

Counters

 


Shift Register

 




After N cycles, the past N values of the input **StateIn** are available in parallel at the output **Q**.

Shift Register with Parallel Load

 

Here, the data can be loaded in parallel using the input D

Scannable flip-flop

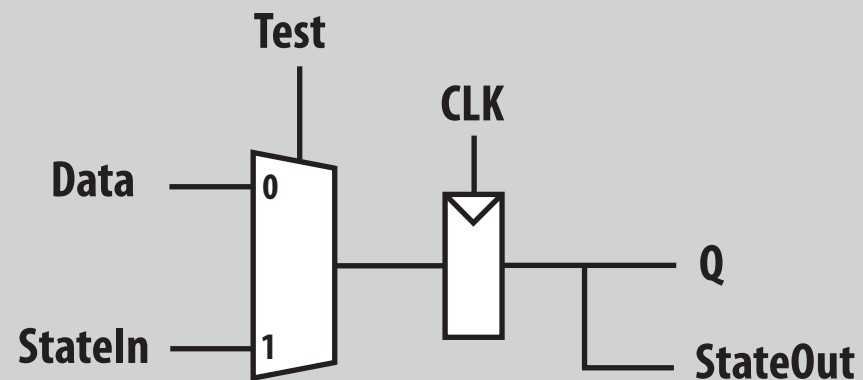 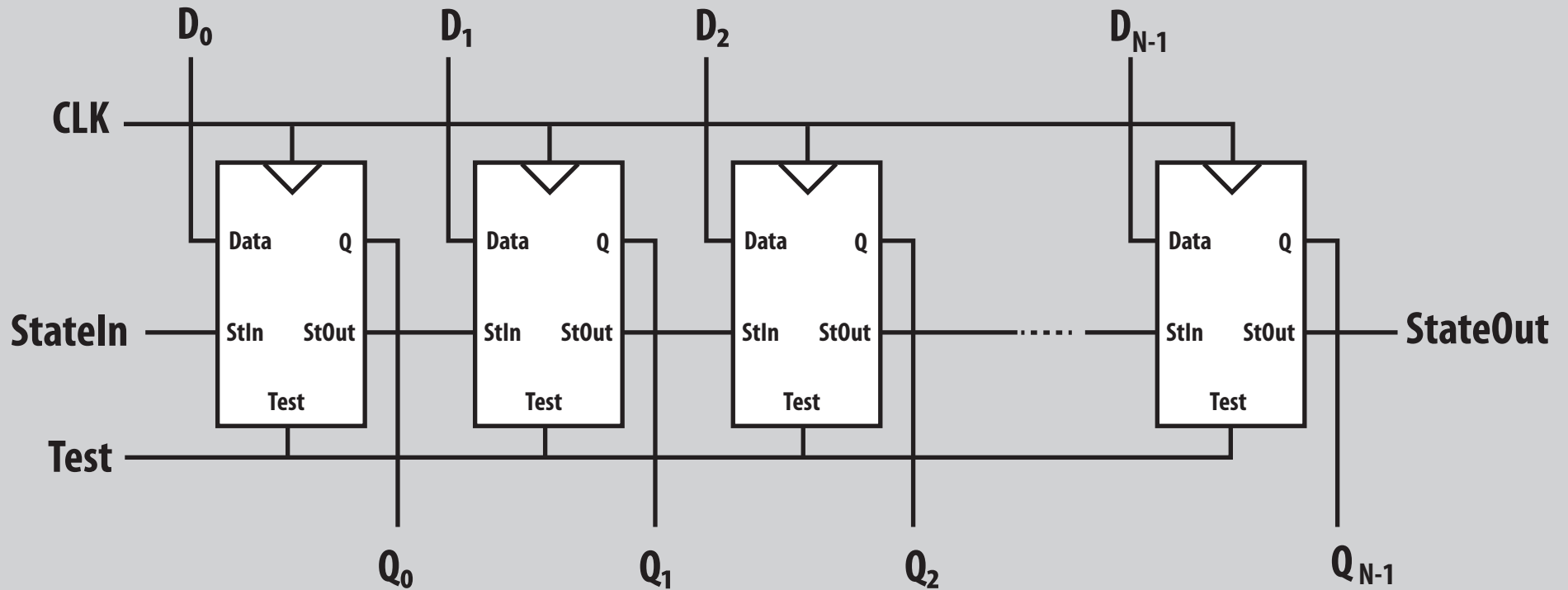

Scan Chains

