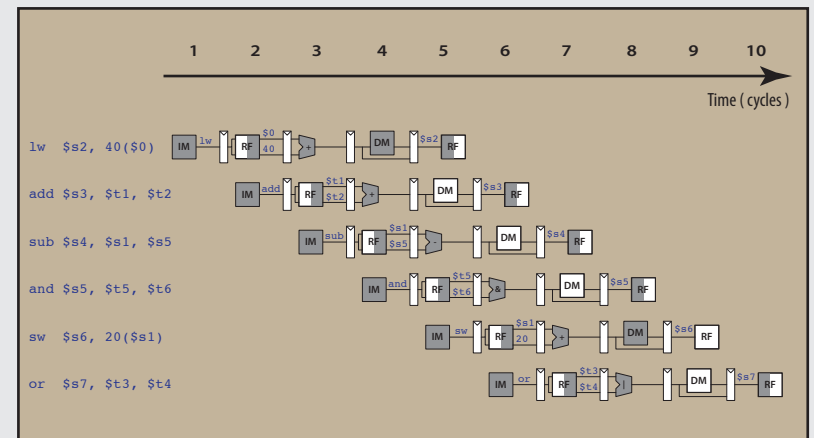



# Computer Architecture

Paul Mellies

## Lecture 16 : Pipelining and dependence hazards



# The pipelined microarchitecture

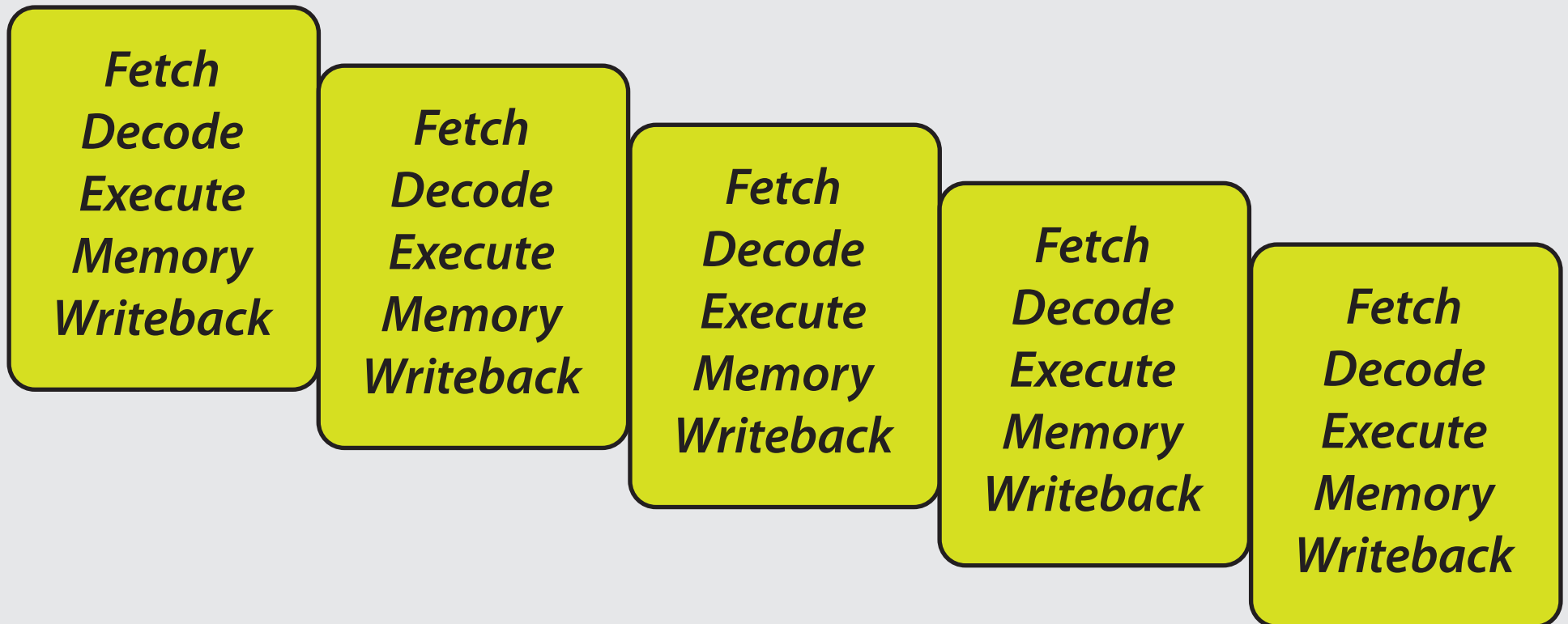

# The five stages of the pipelined microarchitecture



## *Fetch*

The processor reads the instruction from instruction memory.



## *Decode*

The processor reads the source operands from the register file and decodes the instruction to produce the control signals.



## *Execute*

The processor performs a computation with the ALU.



## *Memory*


The processor reads or writes data memory.



## *Writeback*

The processor writes the result to the register file, when applicable.

# The basic principle of pipelining

 

Timing diagrams for single-cycled and pipelined processors

# Exercise

What are the *instruction latency* and *throughput* of

1. the single-cycled microarchitecture
2. the pipelined microarchitecture

described on the previous slide ?

# Solution

What are the *instruction latency* and *throughput* of

1. the single-cycled microarchitecture
2. the pipelined microarchitecture

described on the previous slide ?

**In the case of the single-cycled architecture :**

$$\text{latency} = 250 + 150 + 200 + 250 + 100 = 950 \text{ ps}$$

$$\text{throughput} = 1 \text{ instruction per } 950 \text{ ps}$$

$$= 1.05 \text{ billion instructions per second}$$


**In the case of the pipelined architecture :**

$$\text{latency} = 250 + 250 + 250 + 250 + 250 = 1250 \text{ ps}$$

$$\text{throughput} = 1 \text{ instruction per } 250 \text{ ps}$$


$$= 4 \text{ billion instructions per second}$$

# Abstract view of pipeline in operation

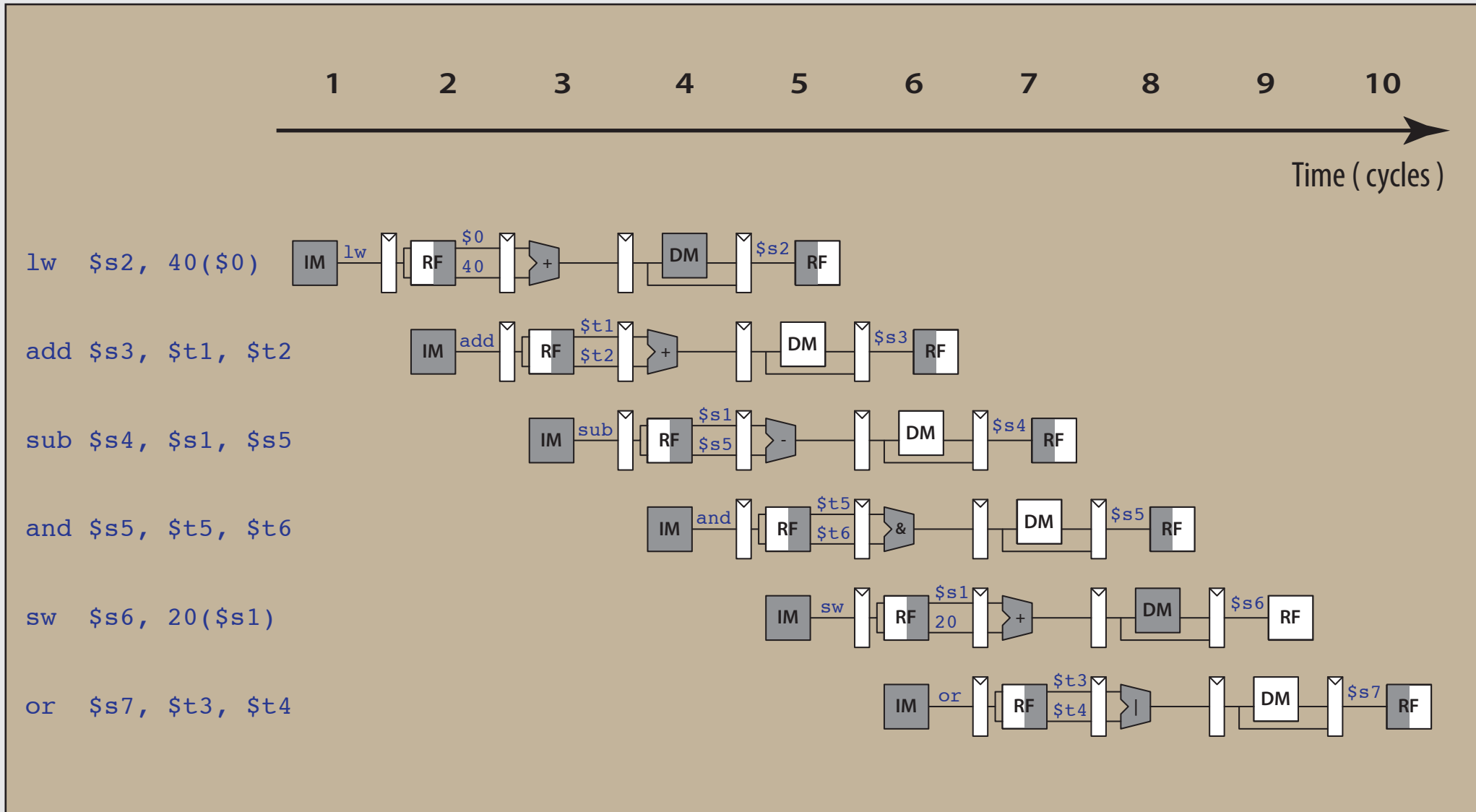


instruction memory (IM), register file (RF) read, ALU execution, data memory (DM), register file (RF) write-back

# Complete single-cycle MIPS processor

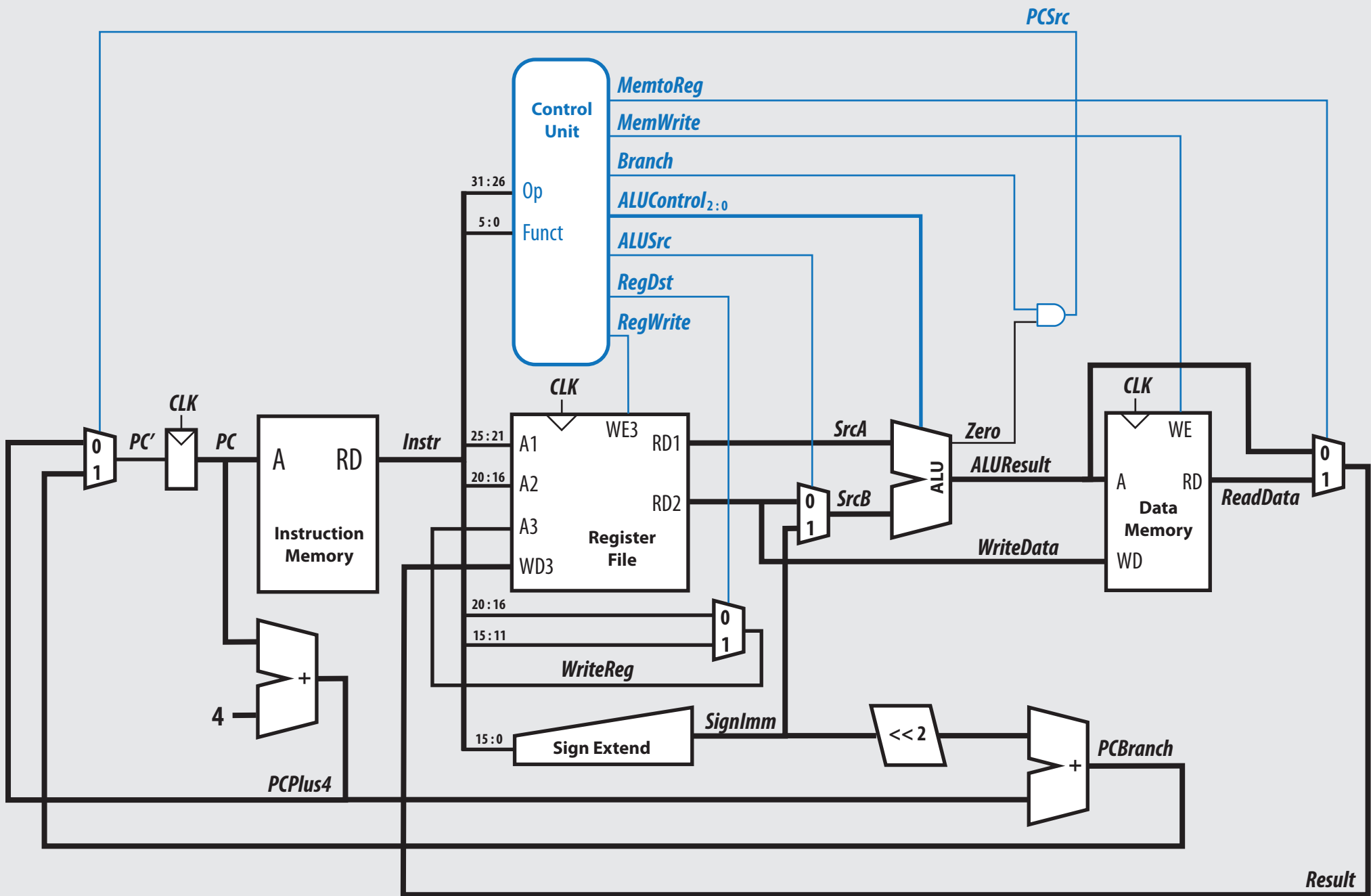





# Complete single-cycle MIPS processor

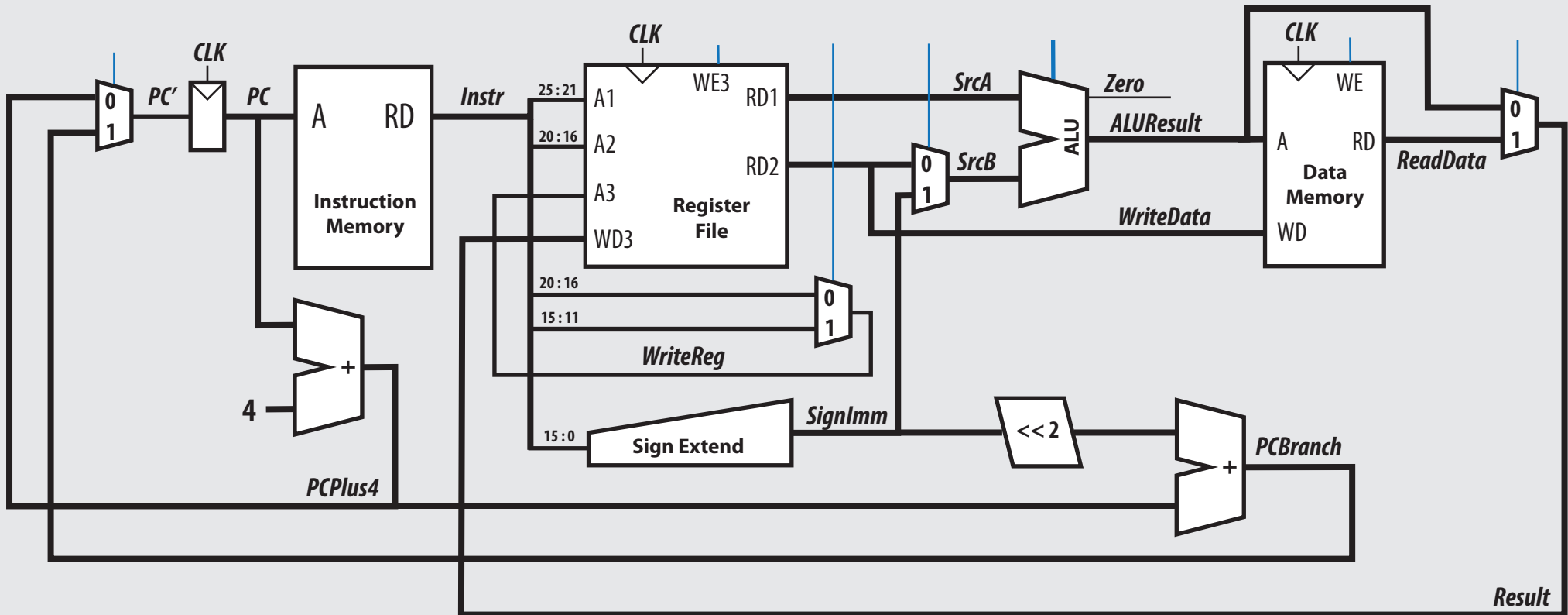

# Single-cycle datapath

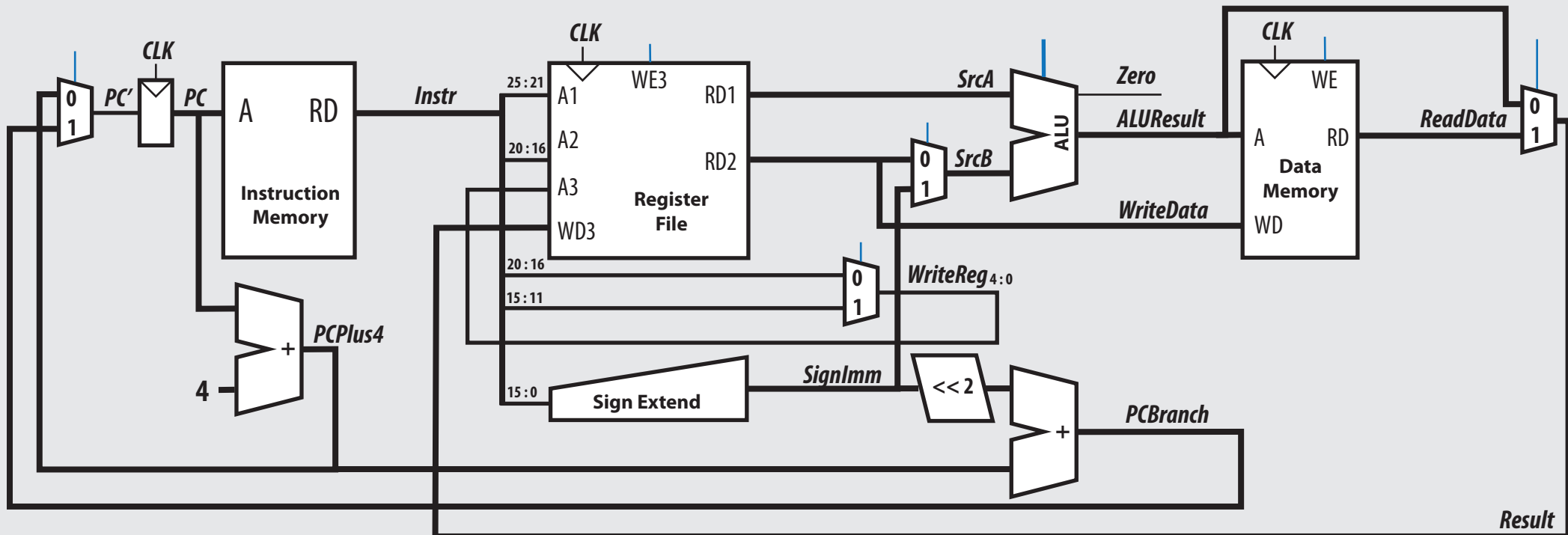


# Pipelined datapath

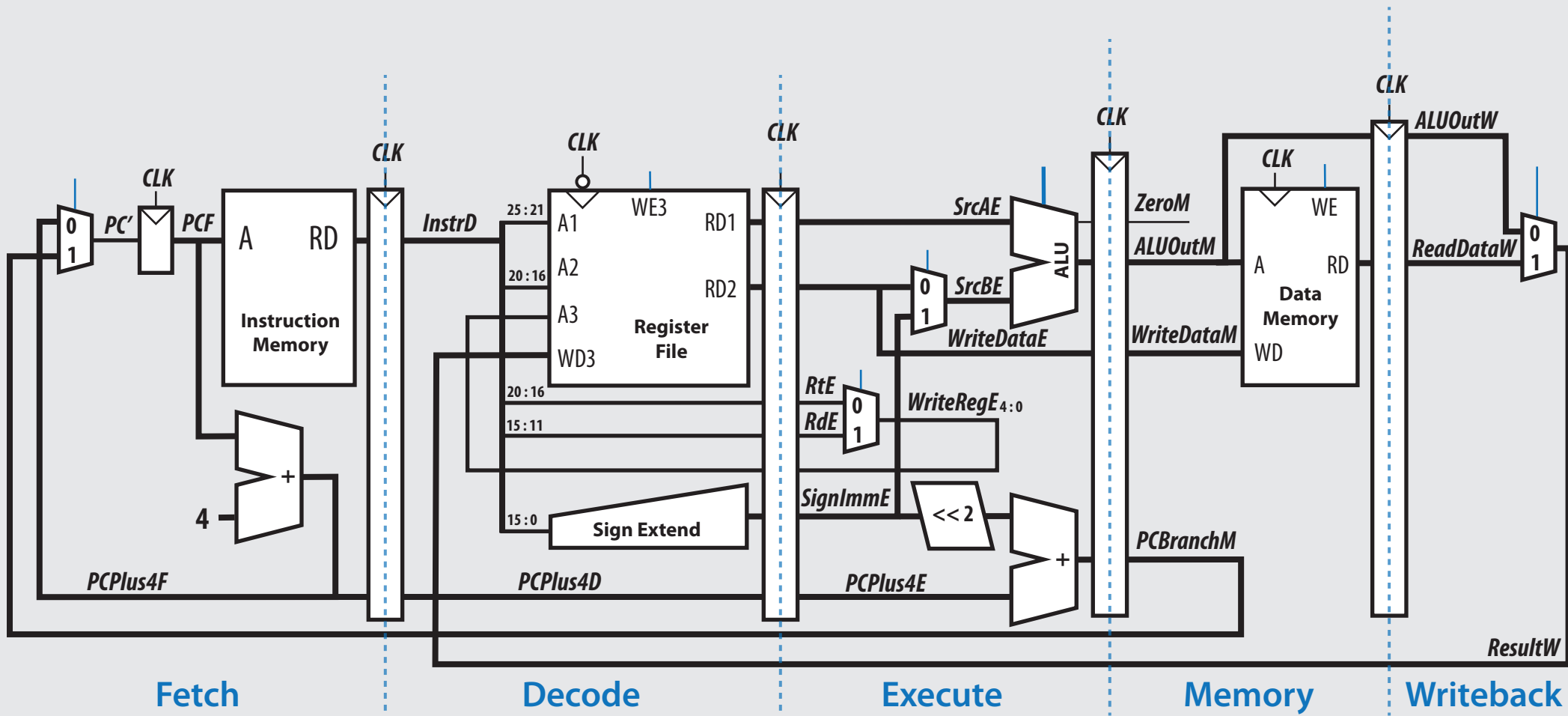


Note the inverter on the clock port of the Register File :  
this ensures that the Register File writes on the *falling edge* the *CLK* signal

# Corrected pipelined datapath

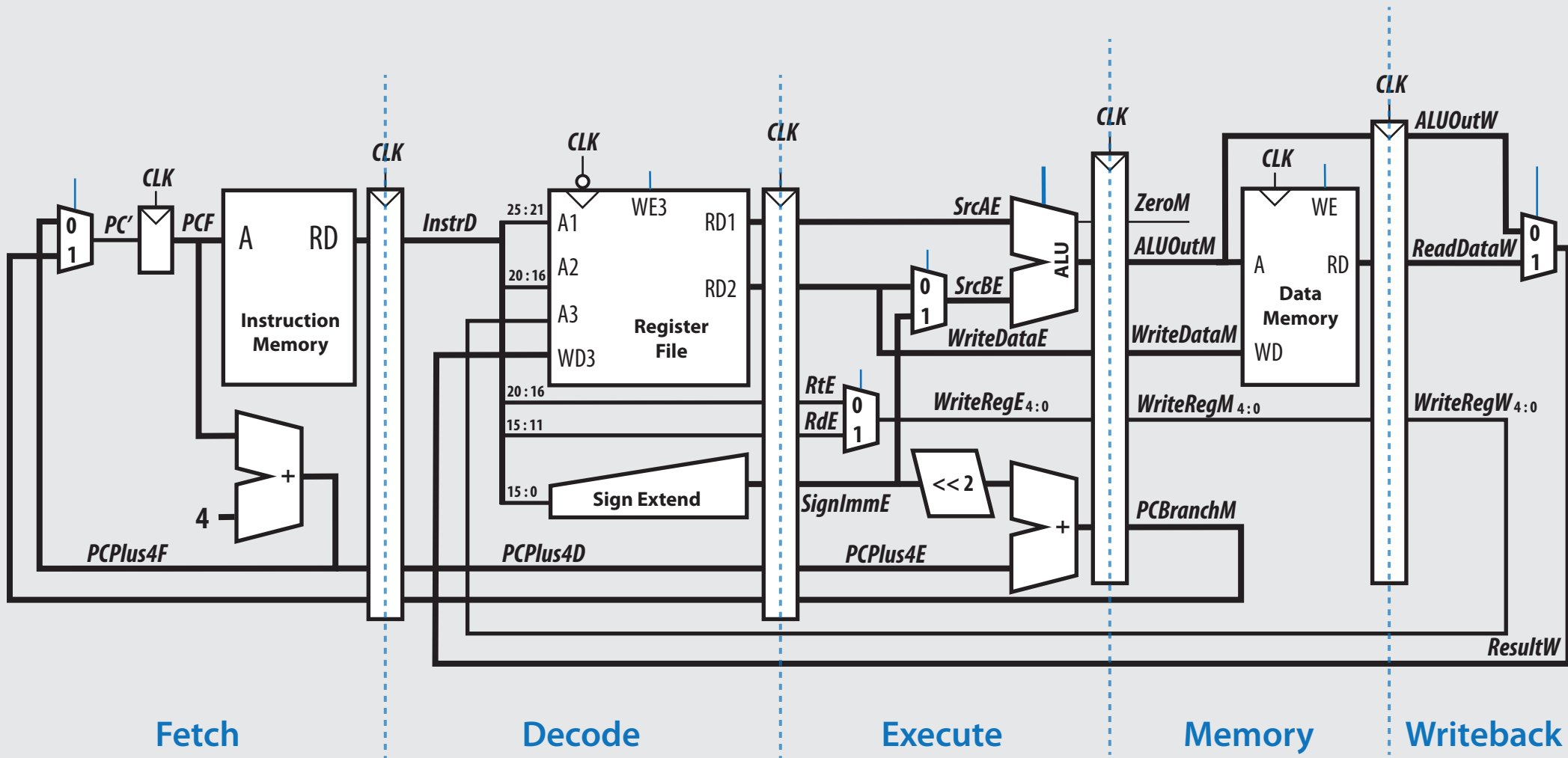

# Pipelined processor with control

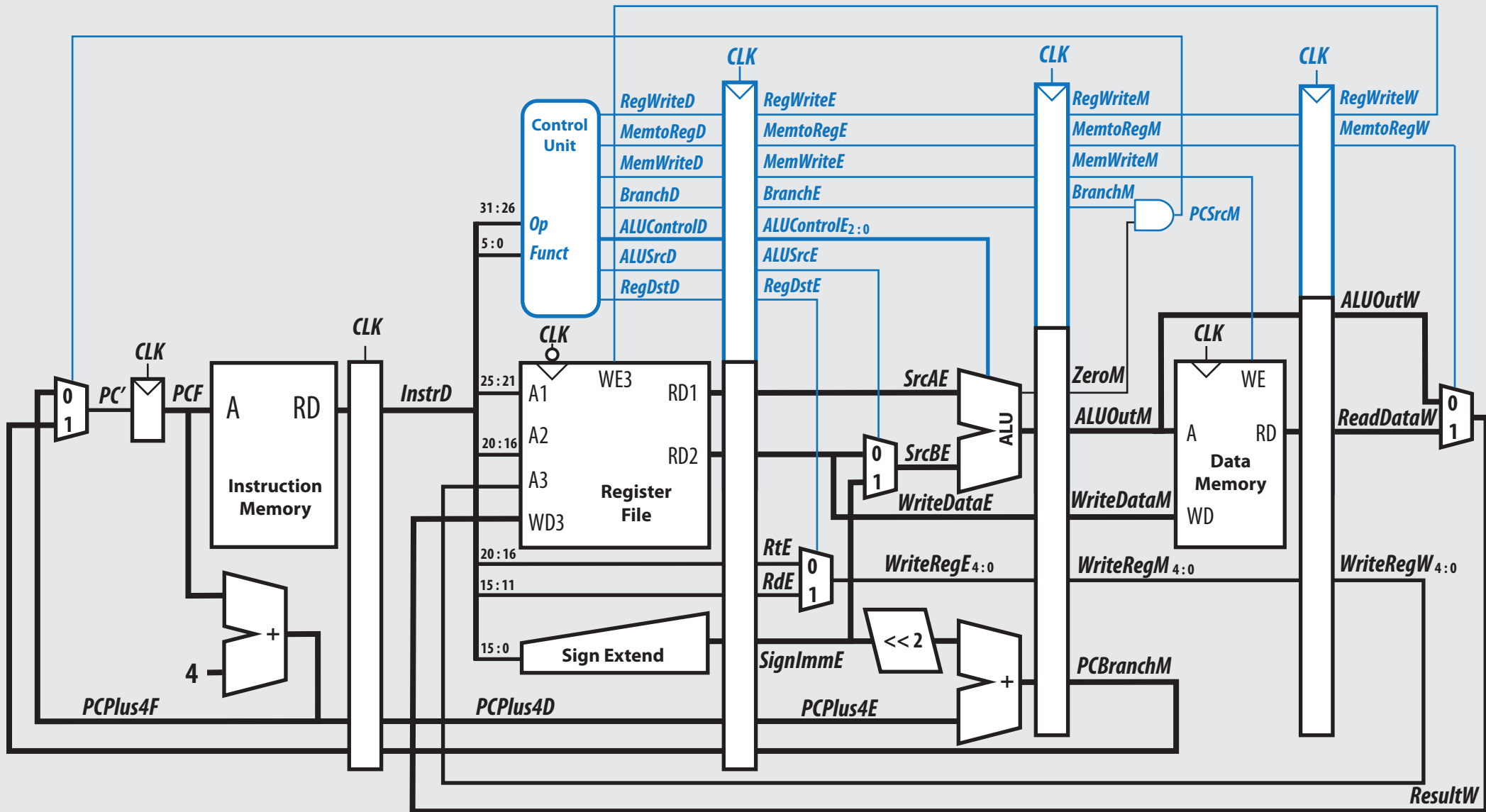

Fetch


Decode

Execute

Memory


Writeback
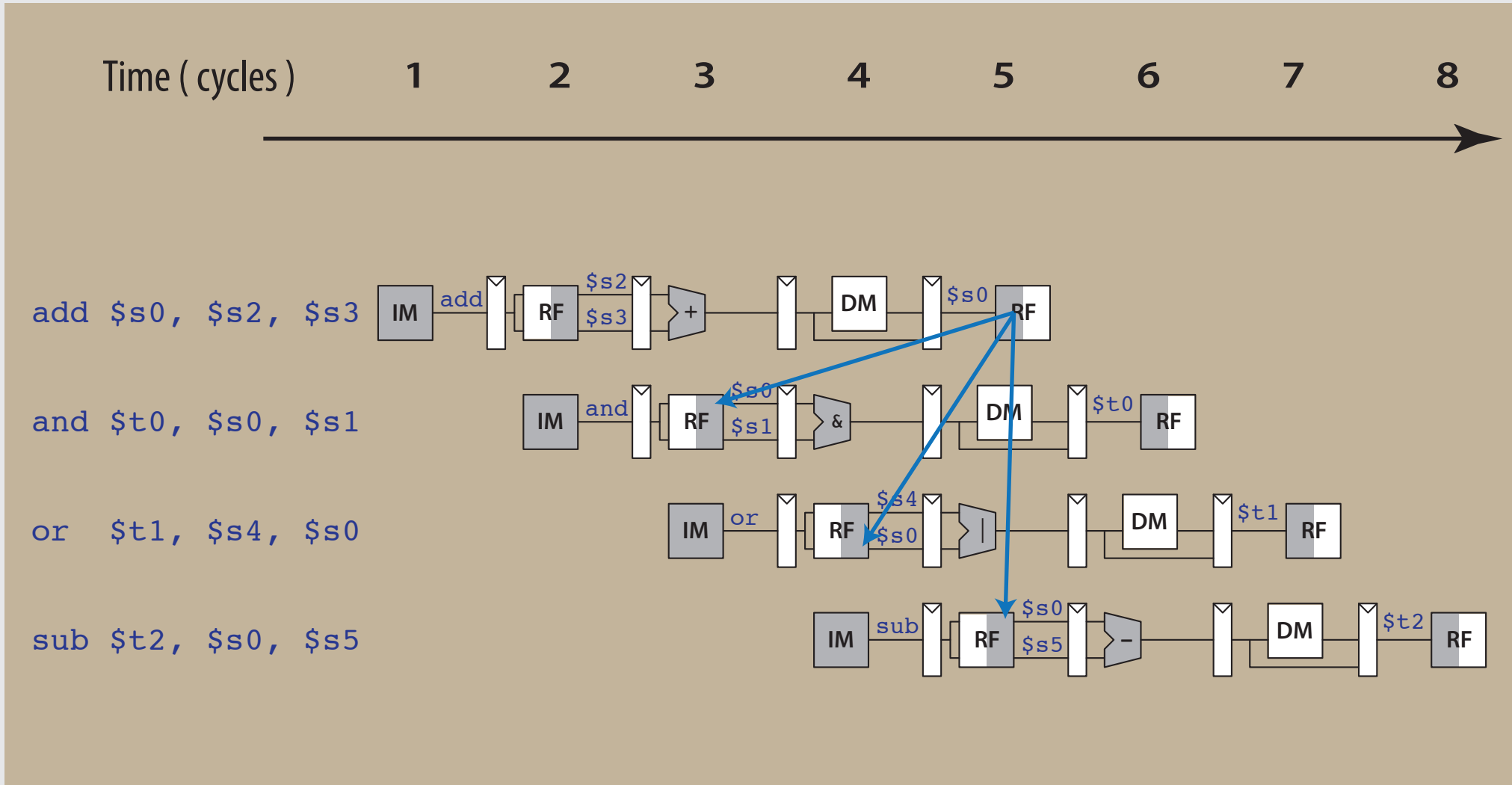
# Abstract pipeline diagram illustrating RAW hazards




RAW = Read After Write
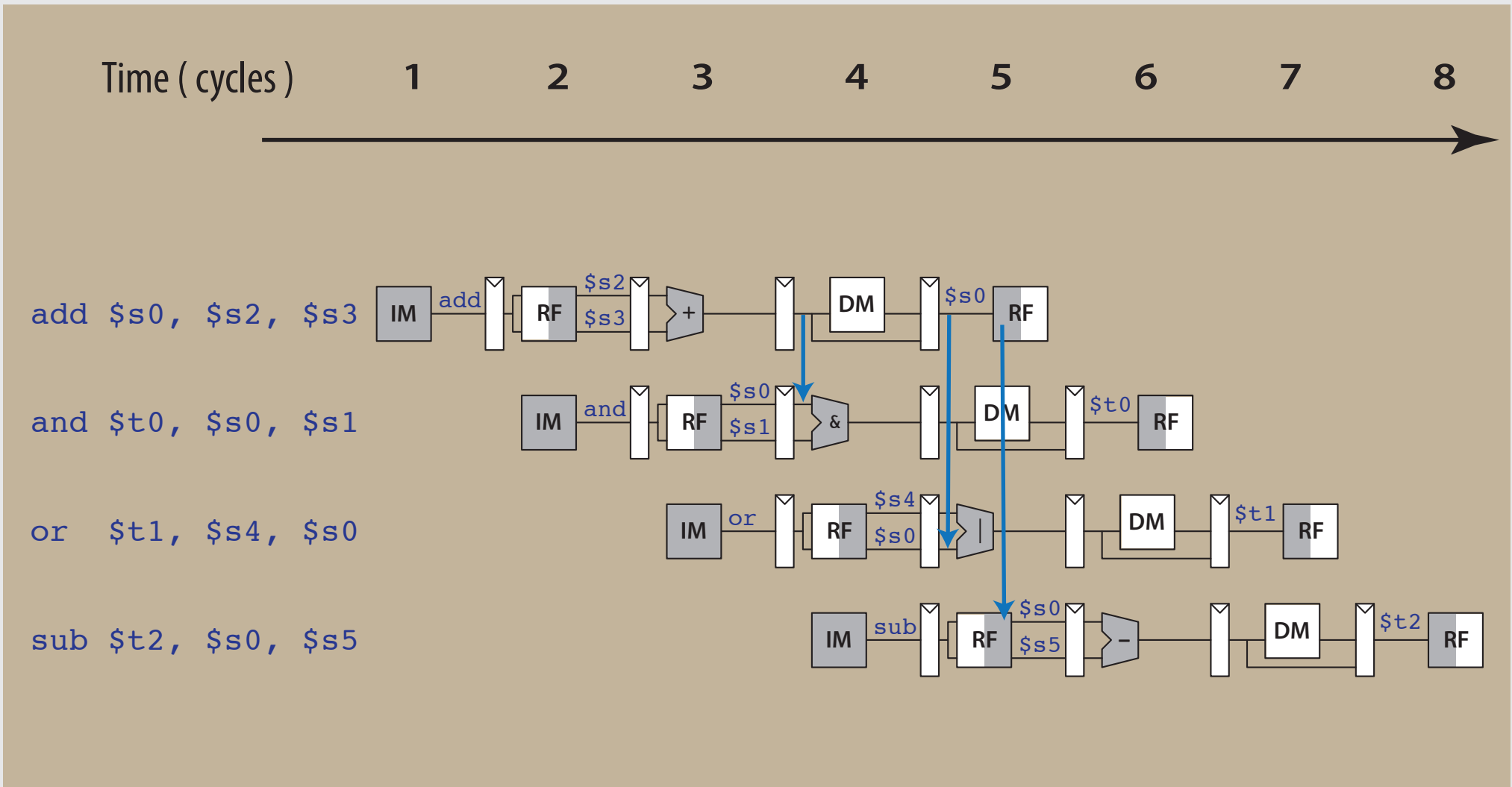
# Abstract pipeline diagram illustrating forwarding




RAW = Read After Write
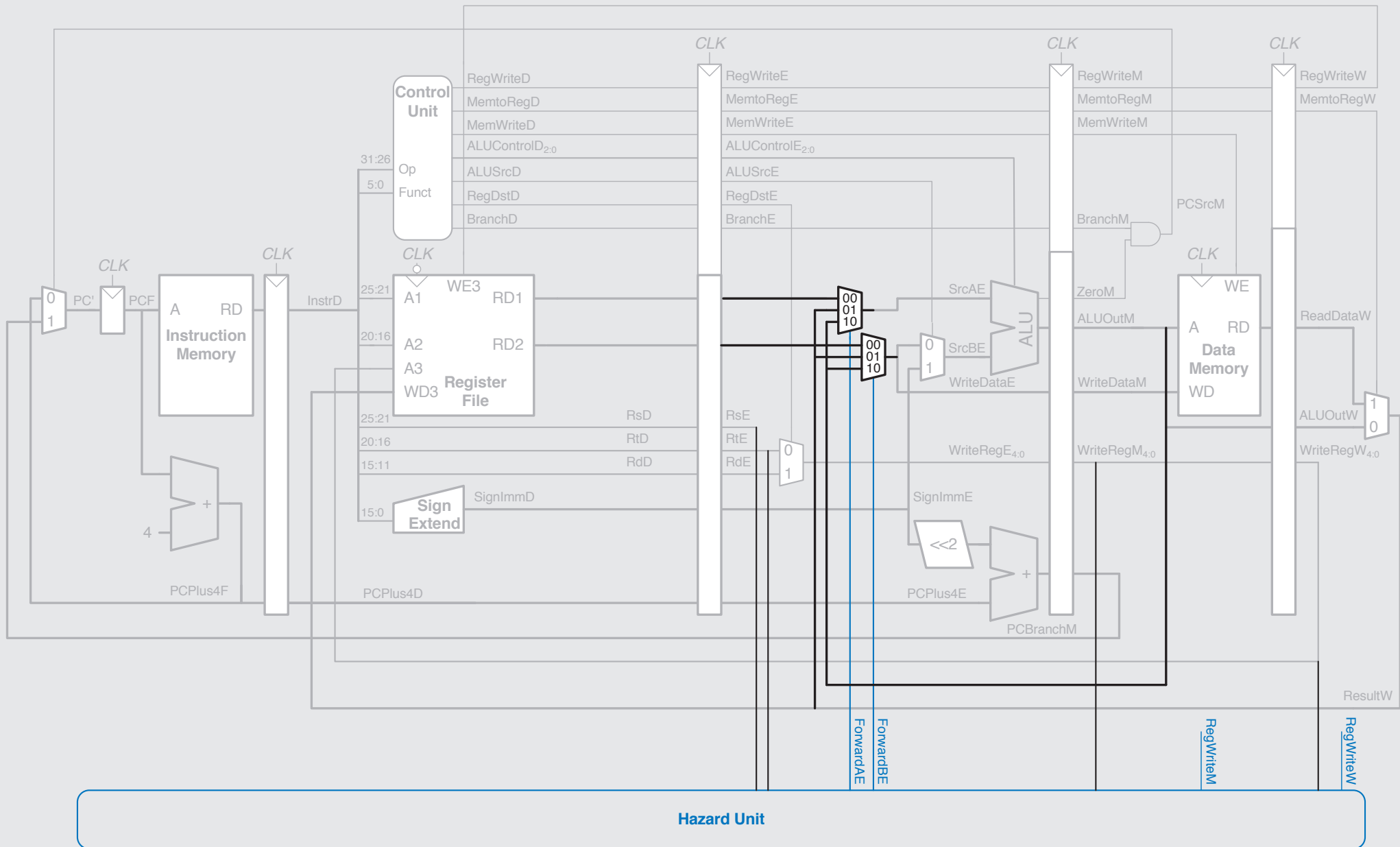
# Pipelined processor with forwarding to solve RAW hazards





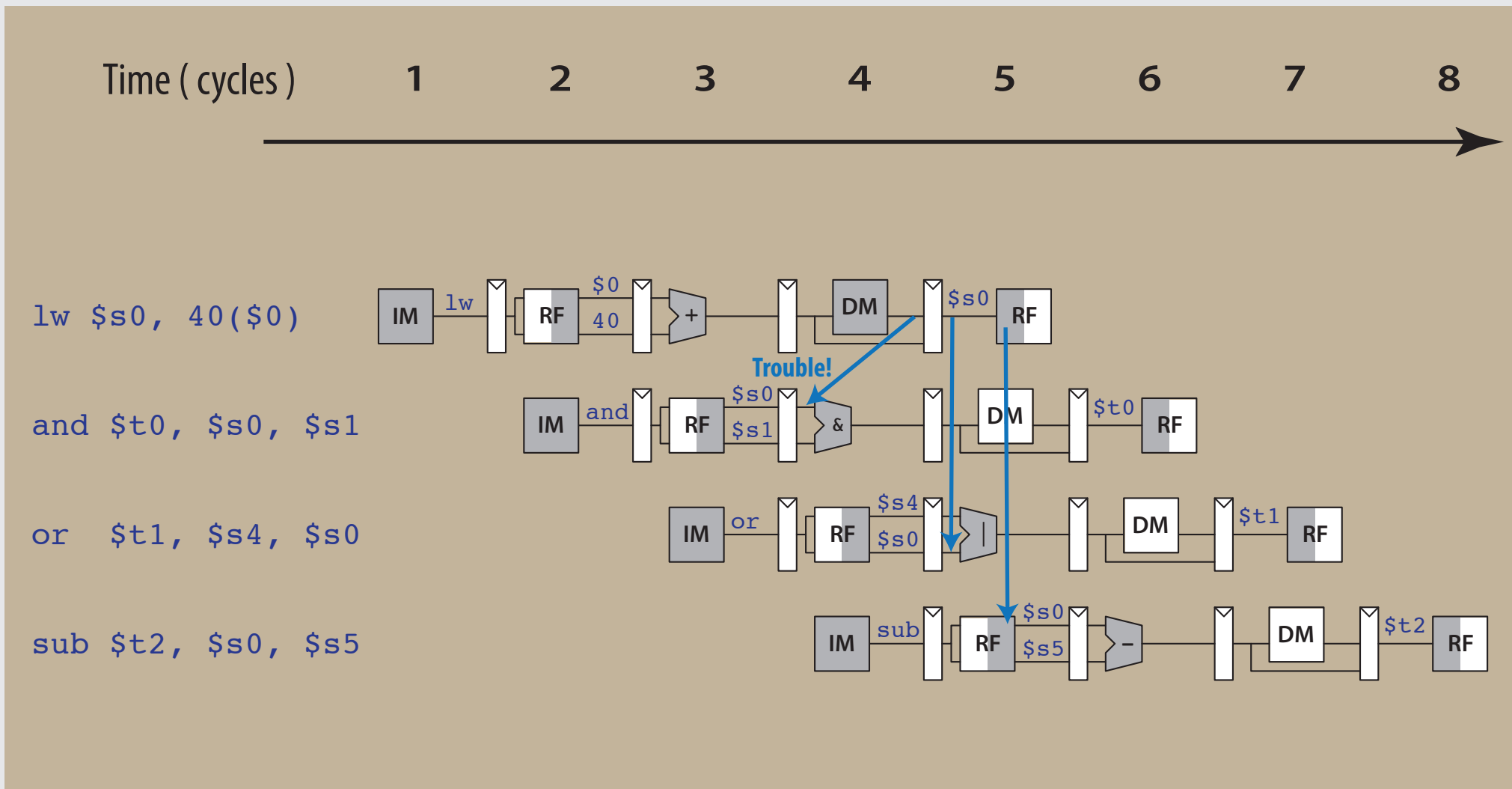
# Abstract pipeline diagram illustrating trouble forwarding `lw`




RAW = Read After Write
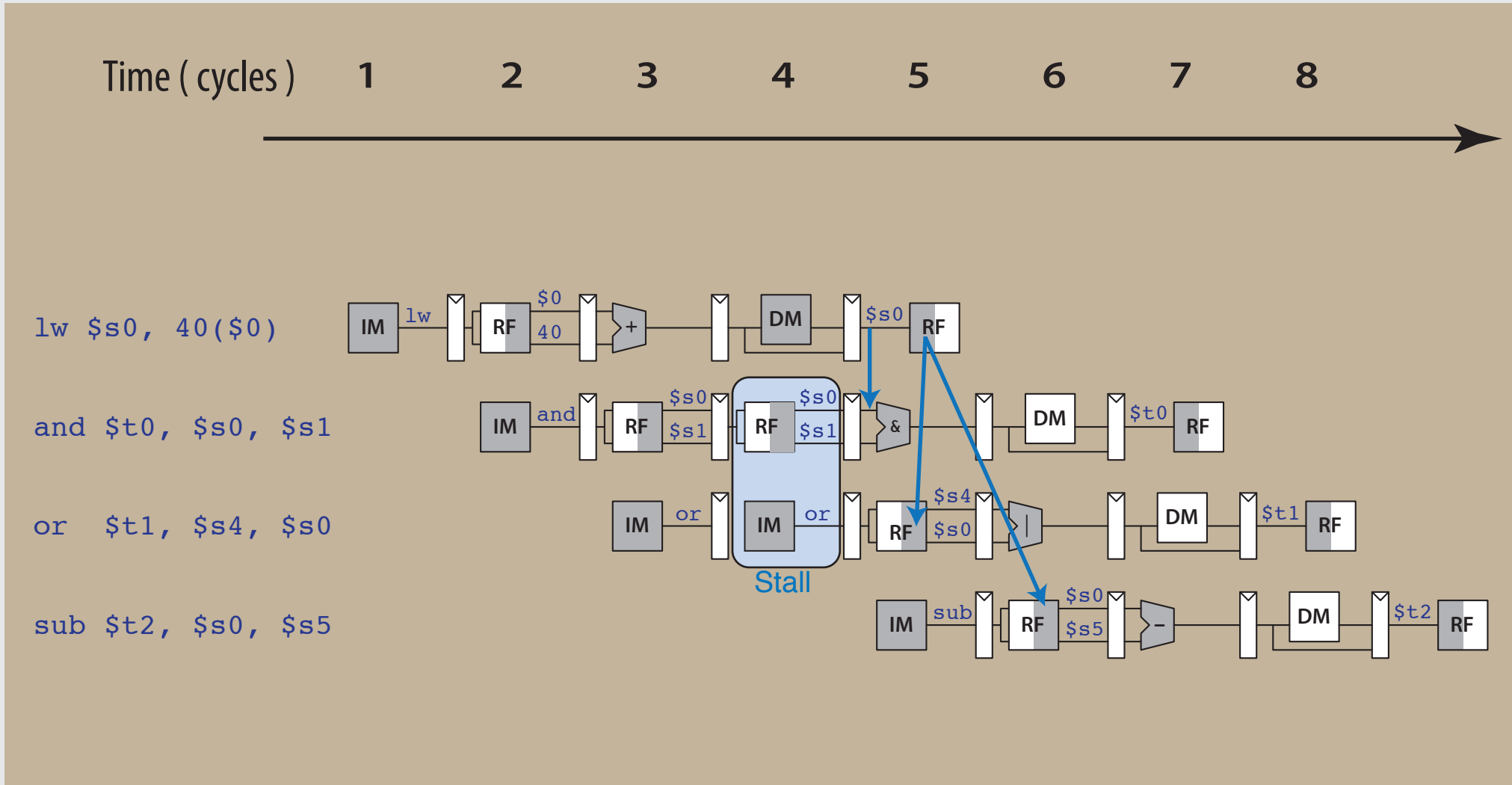
# Abstract pipeline diagram illustrating stalls to solve hazards




RAW = Read After Write

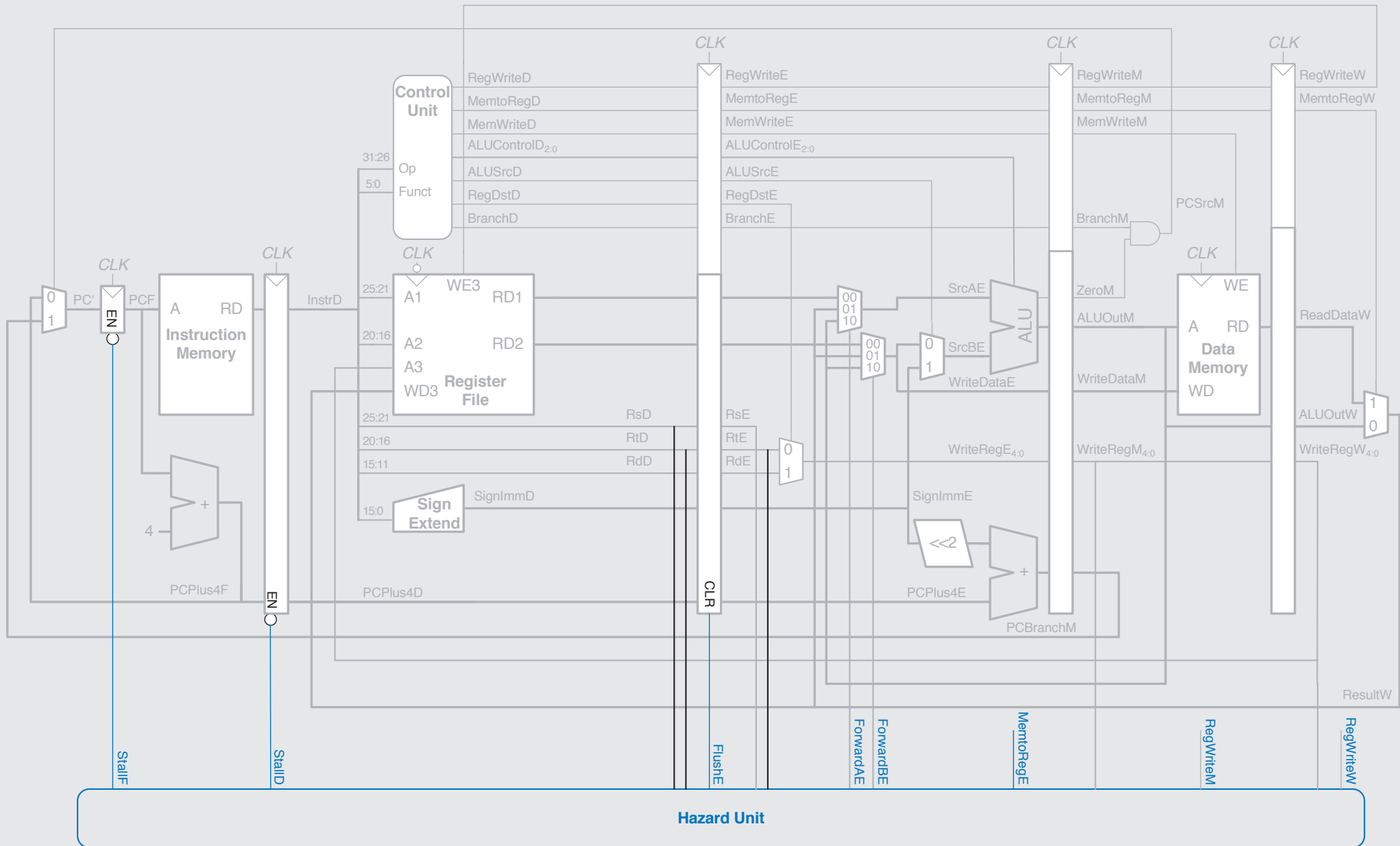
# Pipelined processor with stalls to solve `lw` hazards



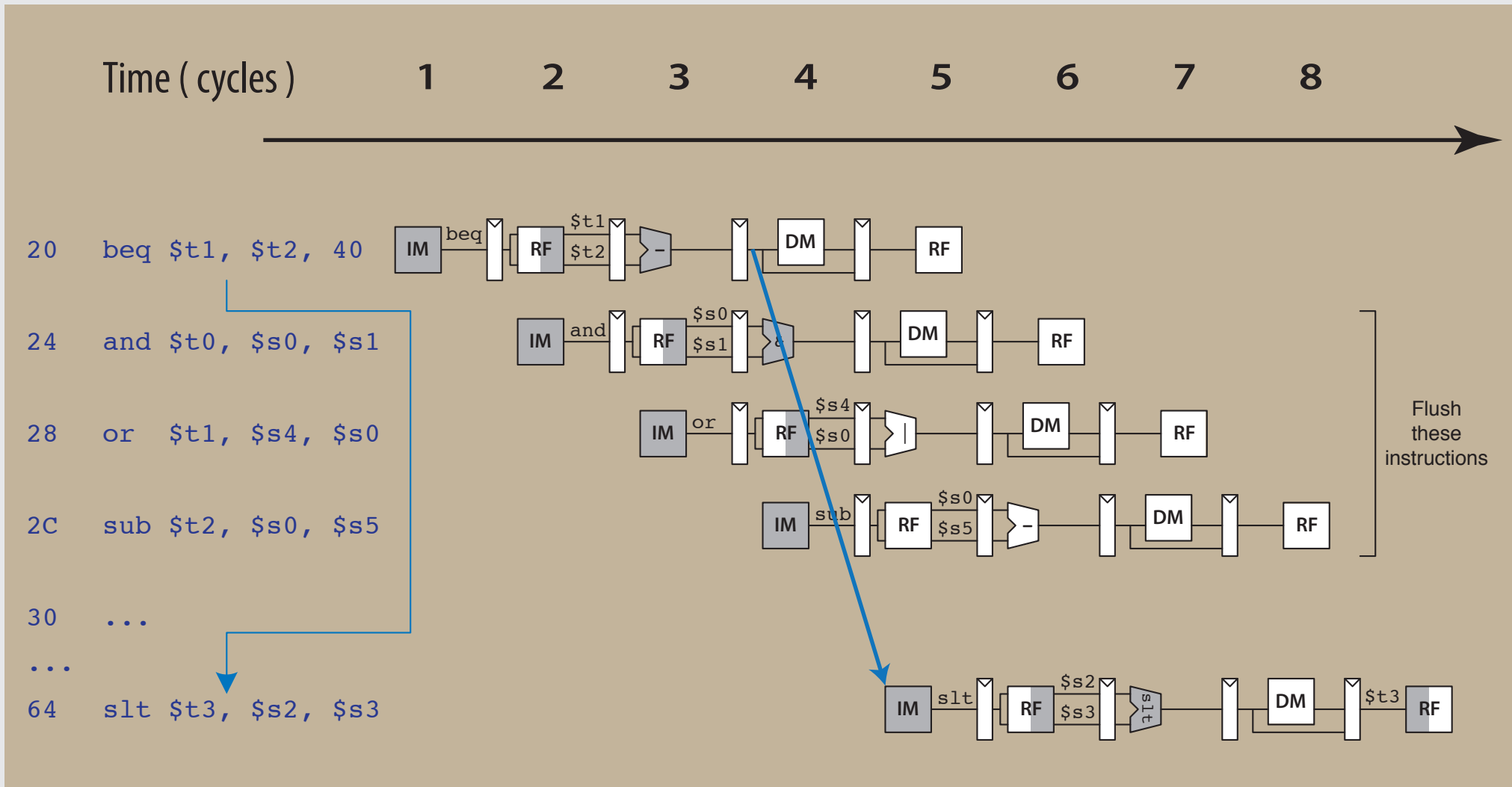
# Abstract pipeline diagram illustrating flushing when a branch is taken


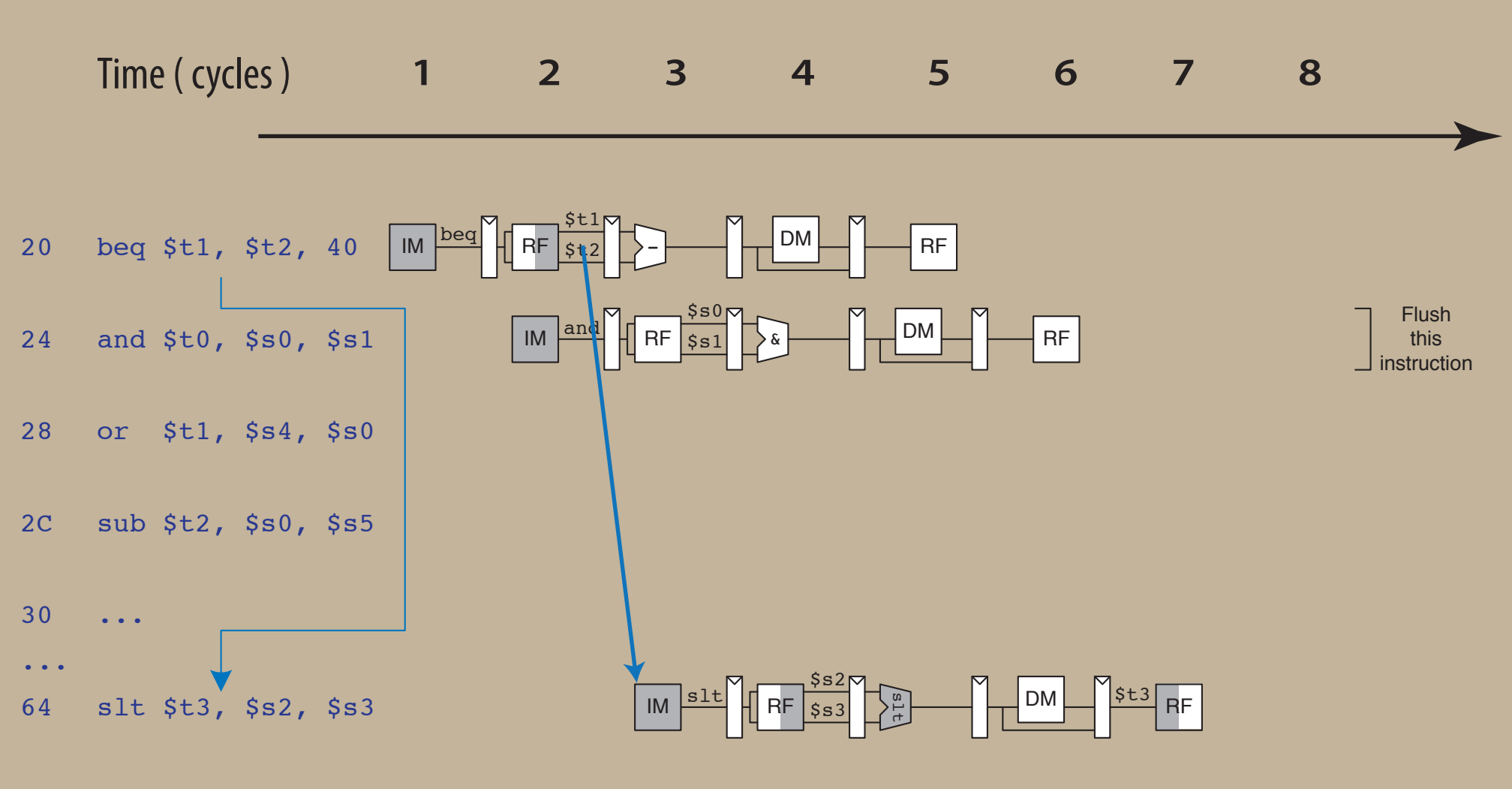
# Abstract pipeline diagram illustrating earlier branch decision


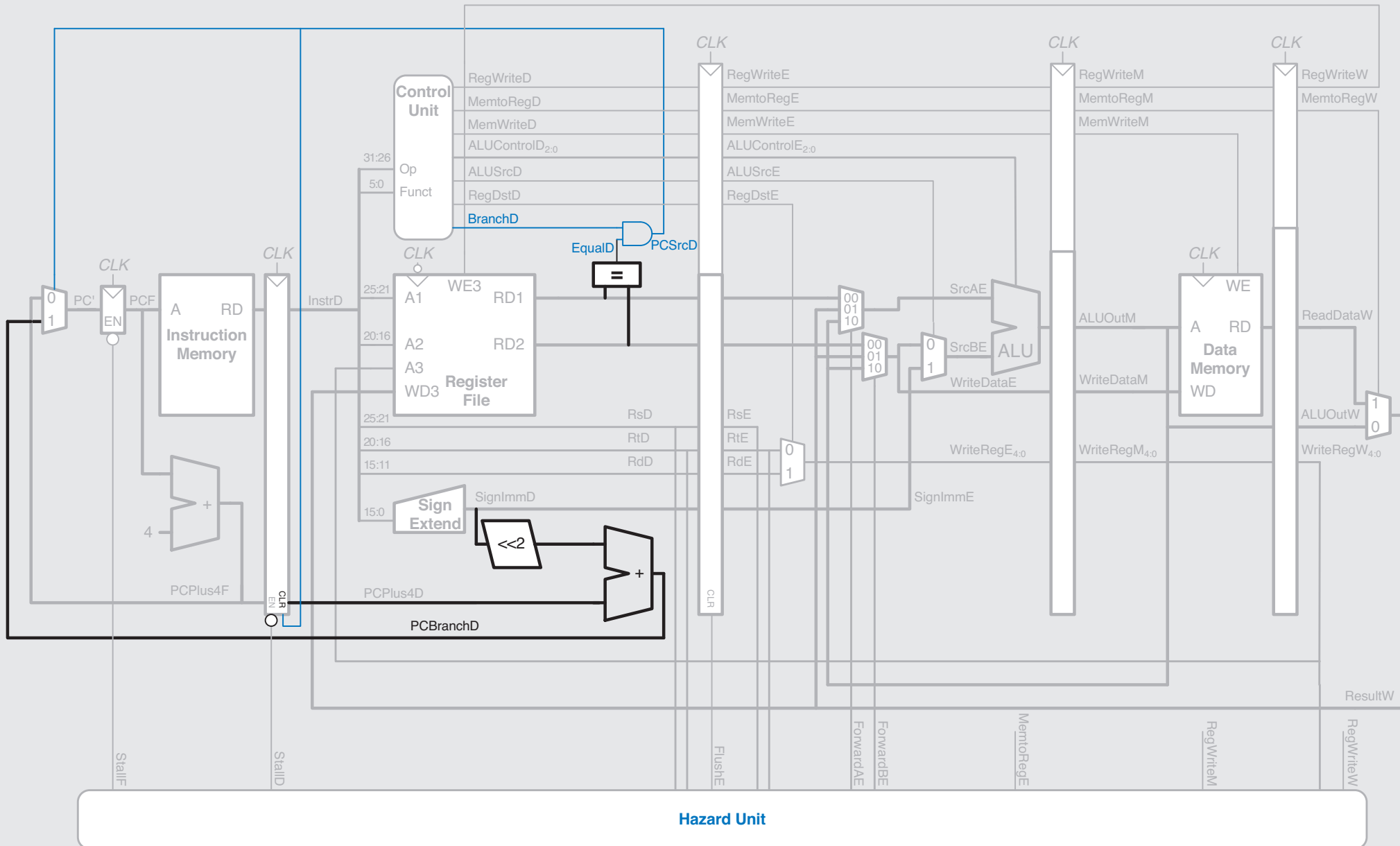
# Pipelined processor handling branch control hazards



# Pipelined processor with full hazard handling

